

PROTOKOLL

for laboratory practice

Oscillator

HTL
St. Pölten

EL

Gruppe / Klasse	Protokollführer	Unterschrift:
5 / 4AHELS	Andreas Böhm	
Übungs- / Abgabedatum	Mitarbeiter	Unterschrift:
11.3.2014 18.3.2014	Thomas Asch	
Lehrer	Mitarbeiter	Unterschrift:
Tillich	Peter Neunteufl	
Note:	Mitarbeiter	Unterschrift:

Oscillator

VERWENDETE GERÄTE:

Tektonix TDS1001B

Protokoll wurde auf EL-Labor Abgabeordner gespeichert: am: 18.3.2014

Task 1:

Calculate a Phase-Shifting-Oscillator Circuit with an OPV and realize it.

$$f_0 = 1\text{kHz}$$

Asymmetric Source = 10 V.

Circuit:

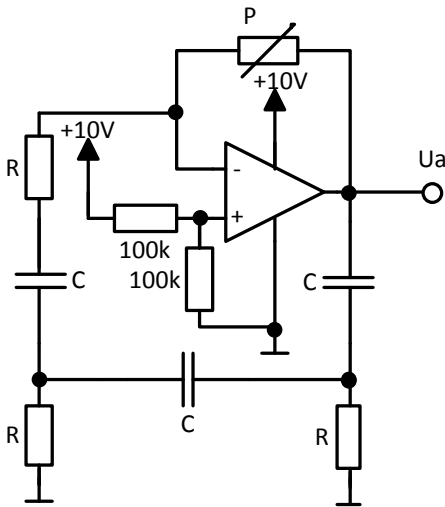


Fig.1: OPV Phase-Shifting Circuit

Calculations:

Assumption:

$$C = 22\text{nF}$$

$$f_0 = 1/(R * 2 * \pi * \sqrt{6} * C)$$



$$\rightarrow R = 1/(f_0 * 2 * \pi * \sqrt{6} * C)$$

$$R = 2,95\text{k}\Omega$$

$$\Rightarrow R = 2,7\text{ k}\Omega$$



$$V = P/R \geq 30!$$

$$\rightarrow P > R * 30 \rightarrow P = 100\text{k}$$

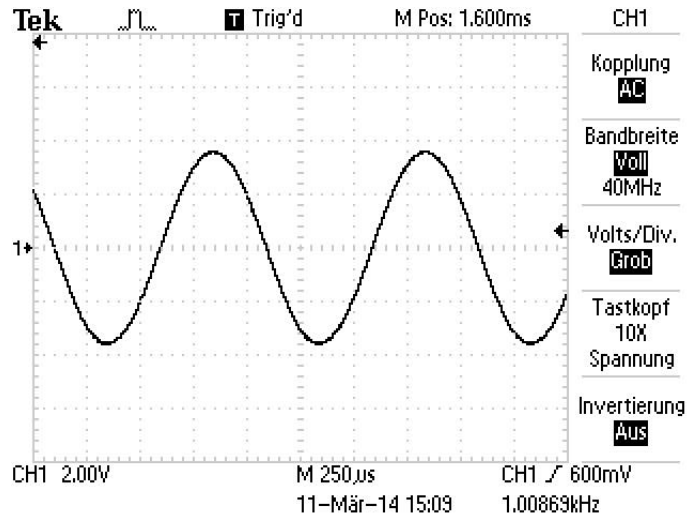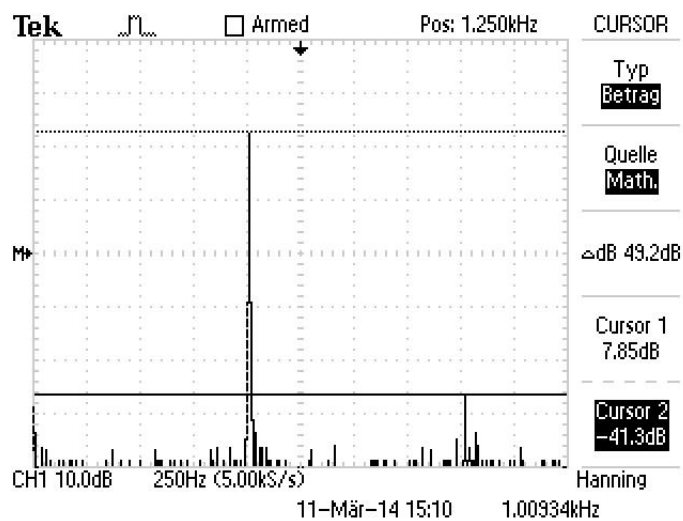Measurement:Fig.2: $U_a(t)$ with good Potentiometer positionFig.3: Spectrum of $U_a(t)$ with good Potentiometer position

$$\text{THD} = -49,2 \text{ dB}$$

$$\Rightarrow \text{THD} = 0,346\%$$

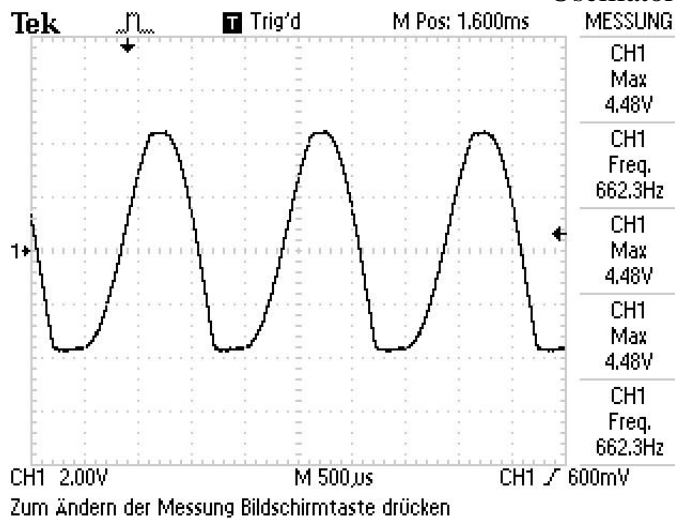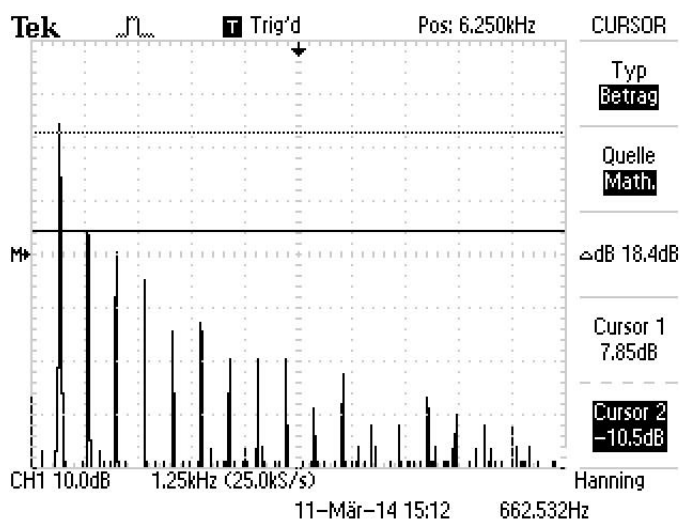Fig.4: $U_a(t)$ with bad Potentiometer positionFig.3: Spectrum of $U_a(t)$ with bad Potentiometer position

$$\text{THD} = -18,4 \text{ dB}$$

$$\Rightarrow \text{THD} = 12,022\%$$

Comment:

In the first measurement the Output Signal $U_a(t)$ had very low harmonics. In the second measurement the THD was up to 12%, that means the difference between first Harmonic and second Harmonic is very low and the sinus isn't perfect.

Task 2:

Calculate a Phase-Shifting-Oscillator Circuit with a Transistor and realize it.

$$f_0 = 1\text{kHz}$$

Asymmetric Source = 12 V.

Circuit:

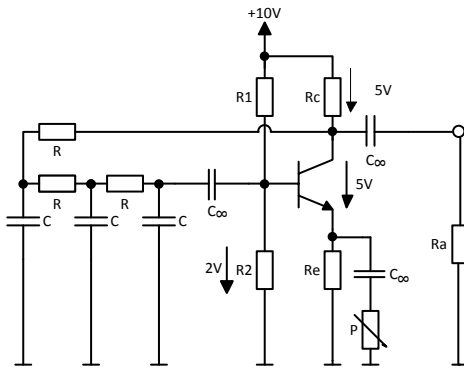


Fig.5: Circuit of Phase-Shifting-Oscillator with a Transistor

Calculation:*Assumption:*

$$C = 22\text{nF}$$

$$I_C = 1\text{ mA}$$

$$f_0 = \sqrt{6/(2 \cdot \pi \cdot C \cdot R)}$$

$$\rightarrow R = \sqrt{6/(2 \cdot \pi \cdot C \cdot f_0)}$$

$$R = 17,72\text{ k}\Omega$$

$$\Rightarrow R = 18\text{k}\Omega$$

$$R_1:R_2 = 8\text{V}:2\text{V} = 4:1$$

Assumption:

$$R_2 = 12\text{ k}\Omega$$

$$R_1 = 4 \cdot R_2 = 48\text{ k}\Omega$$

$$\Rightarrow R_1 = 47\text{ k}\Omega$$

$$R_C = 5\text{V}/I_C = 5\text{ k}\Omega$$

$$\Rightarrow R_C = 4,7\text{ k}\Omega$$

$$R_E = 2\text{V}/I_C = 2\text{ k}\Omega$$

$$\Rightarrow R_E = 1,8\text{ k}\Omega$$

Comment:

Also, through the help of the teacher, the build circuit didn't oscillate. A problem could be the calculation, because there is no or rather a too low Voltage between the Base and the Emitter of the Transistor.