

Documentation

to HWE exercise

Step-Up Converter

HTL
St. Pölten

EL

Group / Class 7 / 3BHEL	Employee HIRSCH L.	Signature
Delivery date 10 th Jan 2014	Employee HOFSTÄTTER A.	Signature
Teacher Tillich	Employee	Signature
Grade	Employee	Signature

Device Under Test

Step-Up Converter

Used Devices

Nr.	Device	Manufacturer	Type
1.	Power Supply	EMG	18135
2.	Digital Multimeter	TE.Electronic	VA18B
3.	Oscilloscope	Tektronix	TDS 1001B
5.	Function Generator	HAMEG	HM8030-6

1 Contents

1	CONTENTS.....	2
2	TASKS.....	3
3	BASIC CONCEPT OF A STEP-UP CONVERTER	3
3.1	MOSFET.....	4
3.2	NE555 AS AN ASTABLE MULTIVIBRATOR.....	4
4	DIMENSIONING AND CALCULATIONS OF THE STEP-UP CONVERTER.....	5
4.1	GIVEN VALUES	5
4.2	PERIOD TIME (T).....	5
4.3	PULSE TIME (t_{ON} AND t_{OFF})	5
4.4	INDUCTIVITY (L).....	5
4.5	CAPACITOR (C_5).....	5
4.6	RESISTORS (R_1 AND R_2).....	6
5	STEP-UP CONVERTER WITH FIXED OUTPUT VOLTAGE (18 V)	7
5.1	MEASUREMENT SETUP	7
5.1.1	SIMULTANEOUS MEASURE OF VOLTAGE WITH AN OSCILLOSCOPE	7
5.2	MEASUREMENT RESULTS	8
5.2.1	$u_{C1}(t)$ AND $u_3(t)$	8
5.2.2	COIL	8
5.2.3	MOSFET (DRAIN-SOURCE).....	9
5.2.4	DIODE.....	9
5.2.5	C_5	10
6	STEP-UP CONVERTER WITH REGULATION (12 V – 18 V).....	11
6.1	MEASUREMENT SETUP	11
6.2	MEASUREMENT RESULTS AT 12 V (MINIMUM OUTPUT VOLTAGE)	12
6.2.1	COIL	12
6.2.2	MOSFET (DRAIN-SOURCE).....	12
6.2.3	DIODE.....	13
6.2.4	C_5	13
6.3	MEASUREMENT RESULTS AT 18 V (MAXIMUM OUTPUT VOLTAGE)	14
6.3.1	COIL	14
6.3.2	MOSFET (DRAIN-SOURCE).....	14
6.3.3	DIODE.....	15
6.3.4	C_5	15
7	STEP-UP CONVERTER WITH REGULATION (12 V – 18 V) AND LOAD REGULATION.....	16
7.1	MEASUREMENT SETUP	16
7.2	MEASUREMENT RESULTS	16
7.2.1	INPUT SIGNAL.....	16
7.2.2	OUTPUT SIGNAL	16
8	OPTO-ISOLATOR.....	17
8.1	MEASUREMENT SETUP	17
8.2	MEASUREMENT RESULTS	17
9	REGISTER OF ILLUSTRATIONS	18

2 Tasks

The given task of this project was to develop a step-up- converter, which would amplify an input voltage of **12V up to 18V**. The frequency, which had to be used, was 110 kHz.

The individual components (e.g. the inductor and the capacitor) had to be calculated with the given values. The inductor had to be coiled according to the calculated value and the capacitor had to be rounded off to fit the next norm value.

All needed values and component were to be dimensioned and calculated.


After the initial setup and dimensioning the Set-Up Converter was built in different versions on the breadboard

Versions and possibilities of the Step-Up Converter:

- Fixed output voltage (18 V)
- Regulation (12 V – 18 V)
 - Load Regulation (dynamic load)
- Regulation (12 V – 18 V) and additional optical isolation of the output
 - Load Regulation (dynamic load)

3 Basic concept of a Step-Up Converter

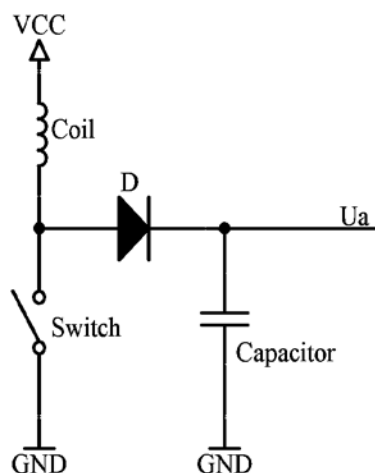All above mentioned versions are all based on the following basic concept. For a very basic and hypothetical Step-Up Converter only 4 components are needed.



- Coil
- Capacitor
- Diode
- Switch (fast switching times)

When the switch gets closed a magnetic field gets inducted in the coil. As soon as the switch is opened up again the coil will do everything to keep the current (that's because the current through an coil doesn't jump). With this current the capacitor is charged.

To prevent discharging of the capacitor a diode is necessary. The diode blocks the current to flow back to the coil. So a higher output voltage is provided.

Figure 1. Basic Concept of a Step-Up

The switch functionality is mostly brought by a transistor or MOSFET which is toggled with a high-frequency rectangular signal. This provides fast switching times on the MOSFET.

In this project a MOSFET, which is connected through an astable multivibrator (NE555 in this case), is used to provide the switch functionality.

3.1 MOSFET

The MOSFET (**M**etal **O**xide **S**emiconductor **F**ield **E**ffect **T**ransistor) can, as mentioned above, be used as a switch.

To implement this, the MOSFETs **Gate** were connected to the NE555s output where the rectangular signal is provided. The **Source** were connected to ground and **Drain** led to the node which splits to the diode and the inductor. This way it functions as the intended switch in Figure 1.

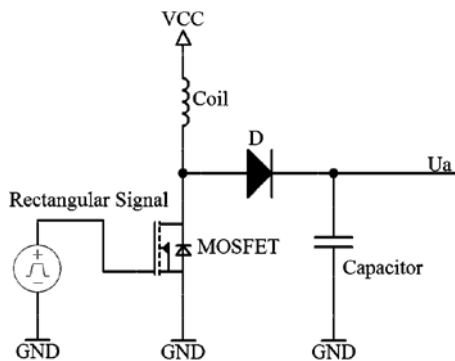


Figure 2. MOSFET as Switch

That's necessary because a MOSFET can handle much more current (between Drain and Source) than the output of a NE555 (e.g. the output current is about 50 mA).

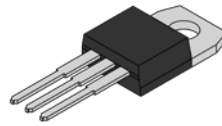


Figure 3. TO-220 case of the MOSFET

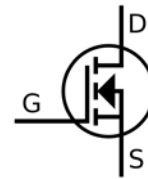


Figure 4. MOSFET circuit symbol

3.2 NE555 as an astable multivibrator

For the rectangular signal which is responsible for switching the MOSFET is provided by a NE555. Its big advantages are that the IC is completely integrated in the circuit. So no additional power supplies or external function generators are needed.

Also a positive aspect is that it is also supplied by a direct current source which could be up to 16 V.

The frequency and pulse width depends on the values for R1, R2 and C1. These three components should be adapted to change the output signals parameters.

Since the frequency determining capacitor was given as fixed value only both resistors need to be calculated based on the other given values in the task.

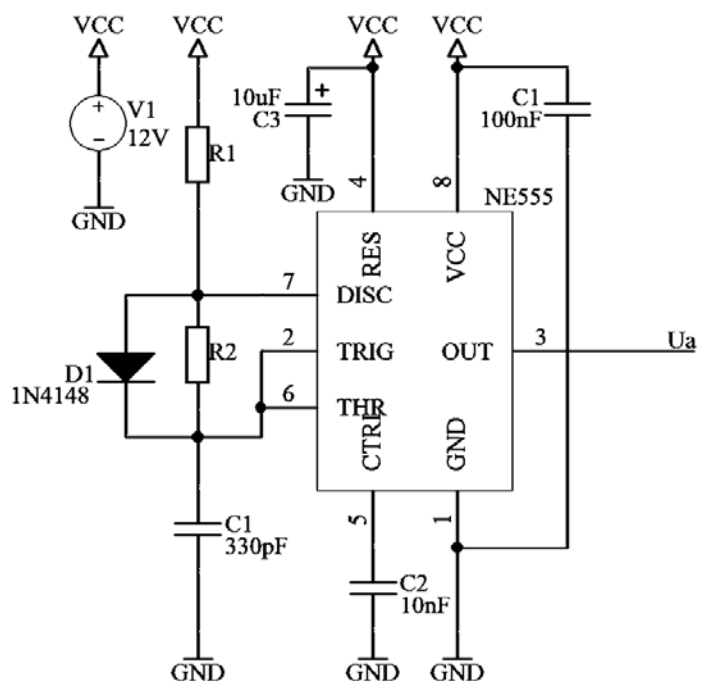


Figure 5. NE555 as an astable multivibrator

4 Dimensioning and Calculations of the Step-Up Converter

4.1 Given Values

The following values were part of the given task and thus set.

$$U_E = 12 \text{ V}; \quad U_A = 18 \text{ V}; \quad P_A = P_E = 3 \text{ W}; \quad f_t = 110 \text{ kHz}$$

4.2 Period Time (T)

Based on the given frequency the period time was calculated.

$$T = \frac{1}{f_t} = \frac{1}{110 \text{ kHz}} \rightarrow T = 9.09 \text{ } \mu\text{s}$$

4.3 Pulse Time (t_{ON} and t_{OFF})

With this result, the time of the positive and negative amplitude produced by the NE555 were reckoned.

$$t_{OFF} = \frac{U_E}{U_A} * T = \frac{12 \text{ V}}{18 \text{ V}} * 9.09 \text{ } \mu\text{s} \rightarrow t_{OFF} = 6.06 \text{ } \mu\text{s}$$

$$t_{ON} = T - t_{OFF} = 9.09 \text{ } \mu\text{s} - 6.06 \text{ } \mu\text{s} \rightarrow t_{ON} = 3.03 \text{ } \mu\text{s}$$

4.4 Inductivity (L)

To calculate the inductivity the maximum current needs to be determined first.

$$\Delta I = 2 * I_E = 2 * \frac{P_E}{U_E} = \frac{2 * 3 \text{ W}}{12 \text{ V}} = \frac{6 \text{ W}}{12 \text{ V}} \rightarrow \Delta I = 0.5 \text{ A}$$

Then it was possible to determine the needed inductivity.

$$L = \frac{U_E * t_{ON}}{\Delta I} = \frac{12 \text{ V} * 3.03 \text{ } \mu\text{s}}{0.5 \text{ A}} \rightarrow L = 72.72 \text{ } \mu\text{H}$$

Which ultimately led to the inductor, which had to be coiled after calculating the amount of windings. The inductance constant of the coil was also part of the task and was given with the amount of $10 \text{ } \mu\text{H}$.

$$N = \sqrt{\frac{L}{A_L}} = \sqrt{\frac{72.72 \text{ } \mu\text{H}}{10 \text{ } \mu\text{H}}} \rightarrow N = 85.28$$

4.5 Capacitor (C_5)

The Capacitor for the step-up converter was calculated with the following formula.

$$C_5 = \frac{\Delta I * t_{OFF}}{2 * 0.18} = \frac{0.5 \text{ A} * 6.06 \text{ } \mu\text{s}}{2 * 0.18} \rightarrow C_5 = 8.416 \text{ } \mu\text{F}$$

To fit the norm standard, the capacitor was normed to the value $C = 10 \text{ } \mu\text{F}$.

4.6 Resistors (R_1 and R_2)

The resistors R_1 and R_2 , which determine the frequency of the astable multivibrator rectangular signal, had to be calculated to fit the allegations.

$$R_1 = \frac{t_{ON}}{\tau * C_1} = \frac{t_{ON}}{0.69 * 330 \text{ pF}} = 13 \text{ k}\Omega \rightarrow R_1 = 12 \text{ k}\Omega$$

$$R_2 = \frac{t_{OFF}}{\tau * C_1} = \frac{t_{OFF}}{0.69 * 330 \text{ pF}} = 26.6 \text{ k}\Omega \rightarrow R_2 = 27 \text{ k}\Omega$$

These resistor values got normed to fit the E12 standard.

5 Step-Up Converter with fixed Output Voltage (18 V)

5.1 Measurement Setup

The following schematic shows the setup for the first measurement, there are also some capacitors for stabilization and smoothing.

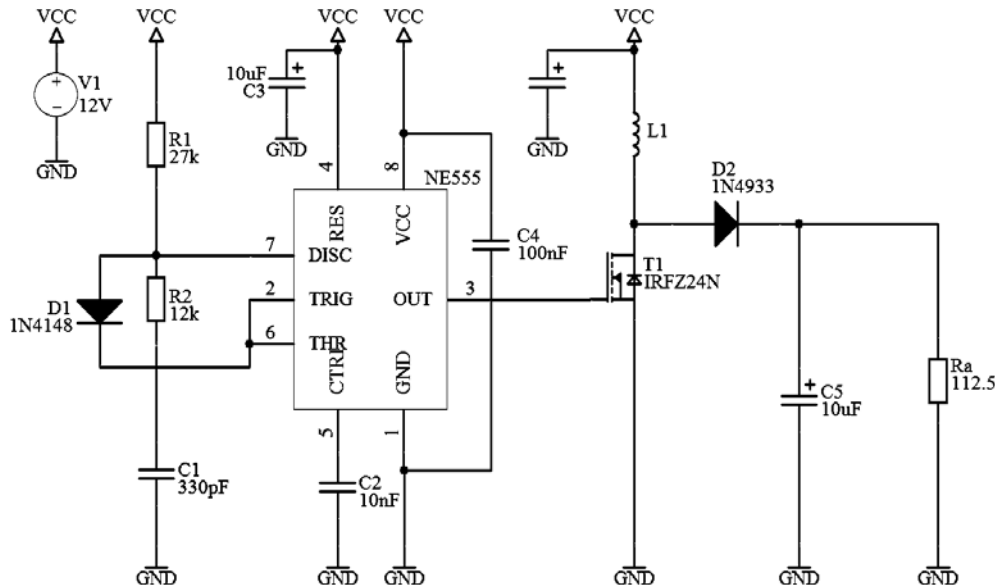


Figure 6. Complete circuit with fixed output voltage

To increase the maximum power of the resistance (R_A) the total resistance consist of 6 individual resistors. These were connected as followed.

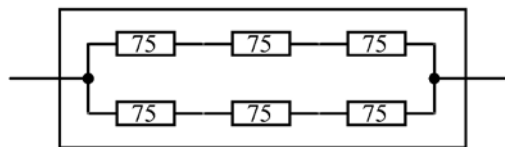


Figure 7. Load resistance (R_A)

With this simple trick the maximum power was increased six-fold. The total resistance is 112.5 Ω

5.1.1 Simultaneous measure of voltage with an oscilloscope

To measure current and voltage at the same time a current-measuring resistor with the amount of 1 Ω was used. The factor of U to I is now exactly 1.

With this trick the voltage signal at the 1 Ω resistor proportional to the current signal.

To measure e.g. the current and voltage of the coil the following setup need to be used.

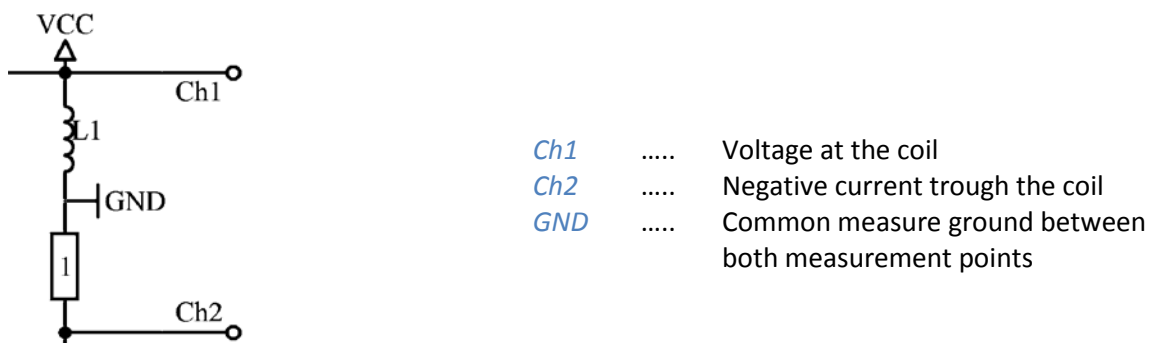


Figure 8. Measurement Setup for oscilloscopes


5.2 Measurement Results

5.2.1 $u_{C1}(t)$ and $u_3(t)$

Ch1: $u_{C1}(t)$

Ch2: $u_3(t)$

Figure 9. Measurements on C1 and NE555 output - fixed output voltage

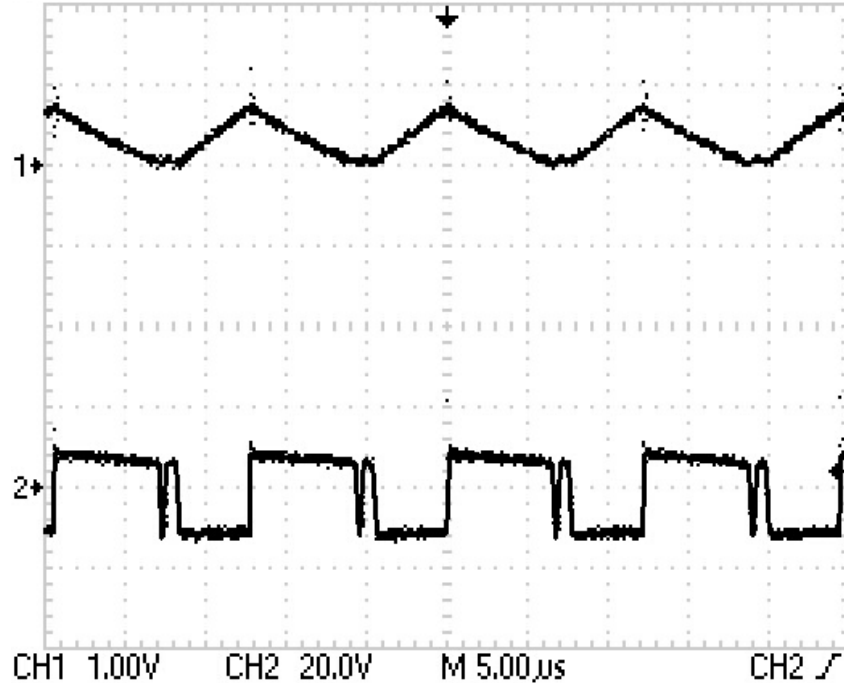


5.2.2 Coil

Ch1: $i_L(t)$

Ch2: $u_L(t)$

Figure 10. Measurements on the coil - fixed output voltage

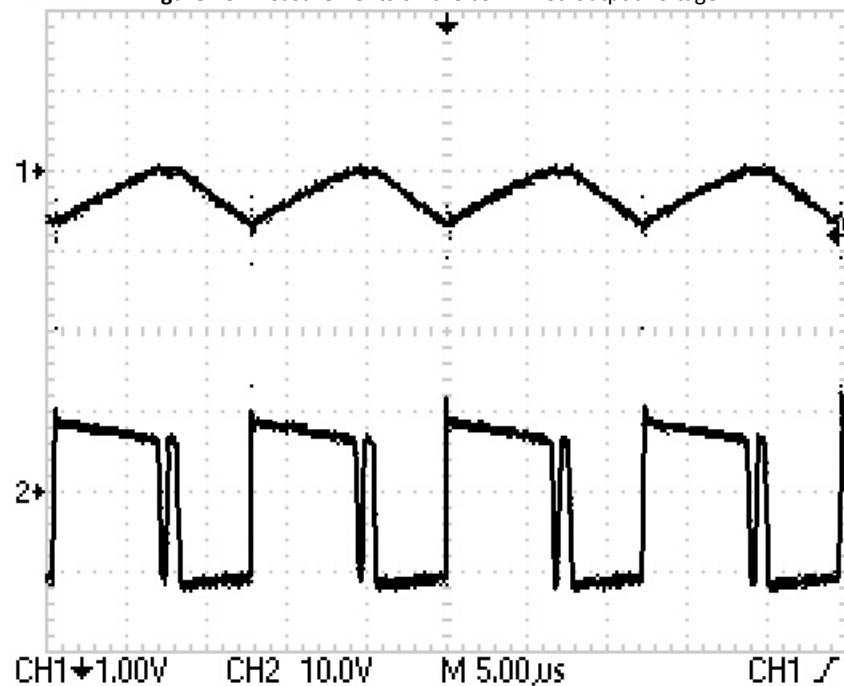


5.2.3 MOSFET (Drain-Source)

Ch1: $i_{DS}(t)$

Ch2: $u_{DS}(t)$

Figure 11. Measurement on the MOSFET (Drain-Source) - fixed output voltage

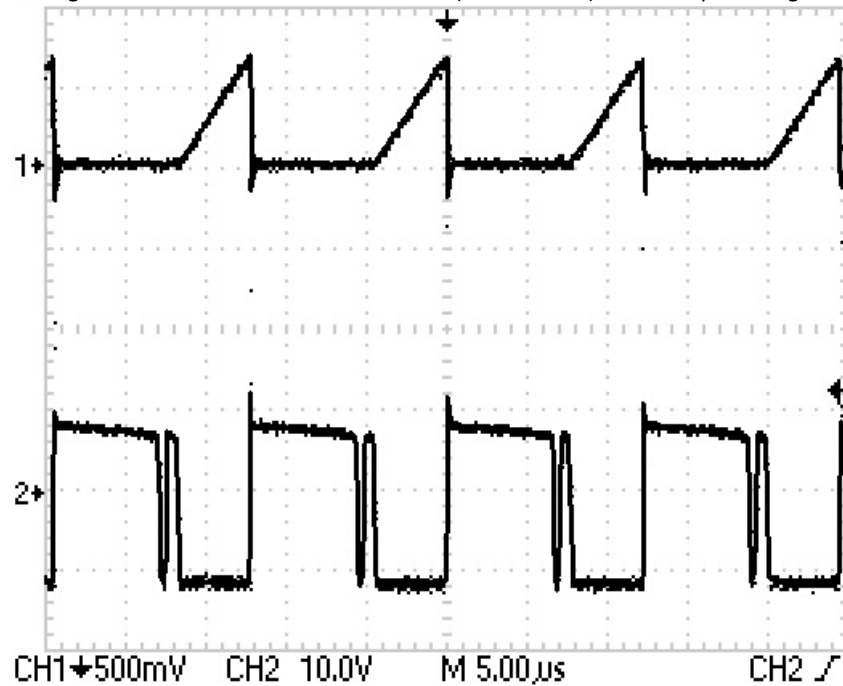


5.2.4 Diode

Ch1: $i_D(t)$

Ch2: $u_D(t)$

Figure 12. Measurement on the diode - fixed output voltage

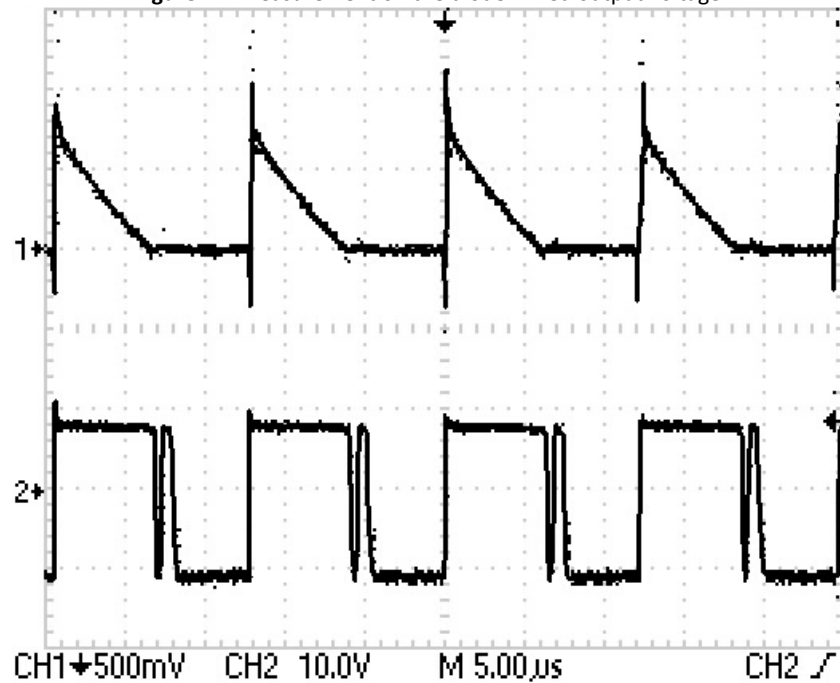


5.2.5 C_5

Ch1: $i_{C5}(t)$

Ch2: $\Delta u_{C5}(t)$

Figure 13. Measurement on C5 - fixed output voltage

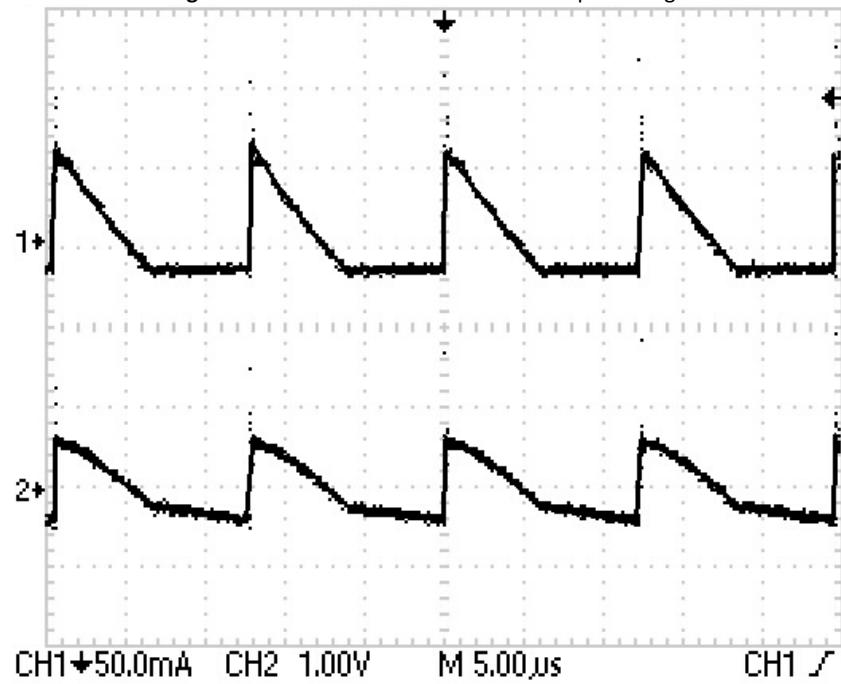

6 Step-Up Converter with regulation (12 V – 18 V)

6.1 Measurement Setup

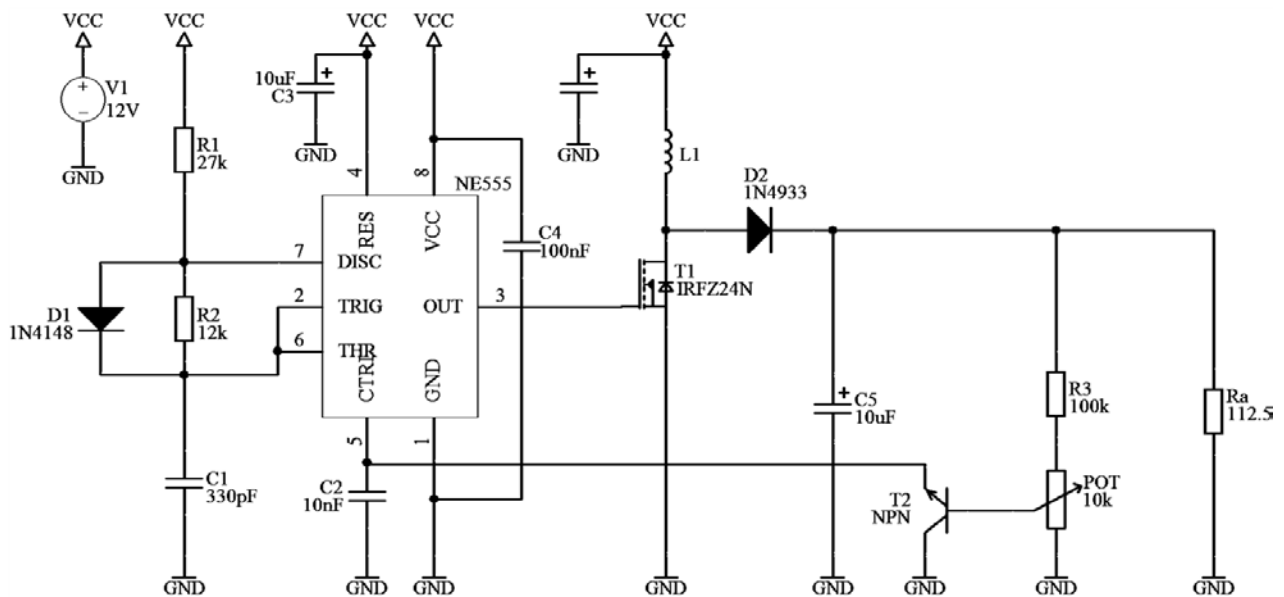


Figure 14. Complete circuit with regulation

With this circuit it is possible to regulate the output voltage from V_{cc} to U_a . In this case the regulation goes from **12 V to 18 V**.


This works because at the current extraction from Pin 5 of the NE555 the pulse width of the converter got shortened. Thereby the output voltage decreases and the switching frequency rises up.

6.2 Measurement results at 12 V (minimum output voltage)

6.2.1 Coil

Ch1: $u_L(t)$


Ch2: $i_L(t)$

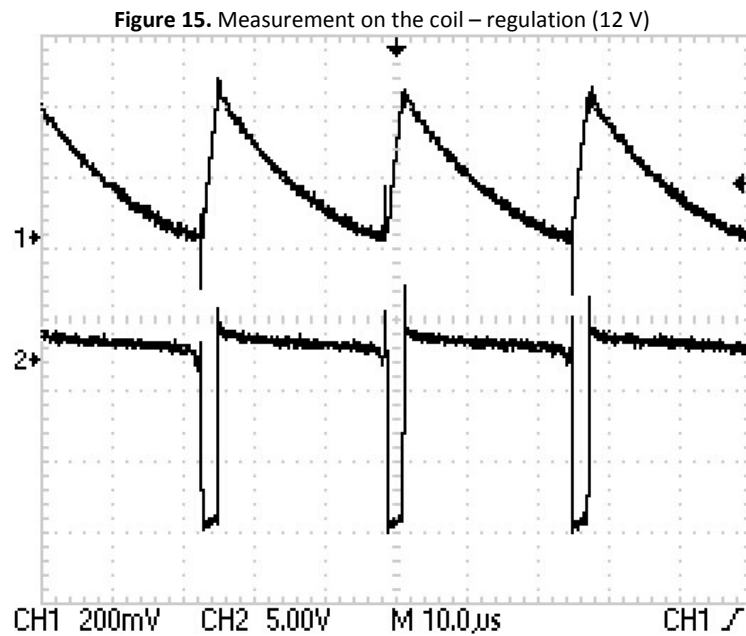

6.2.2 MOSFET (Drain-Source)

Ch1: $u_{DS}(t)$

Ch2: $i_{DS}(t)$

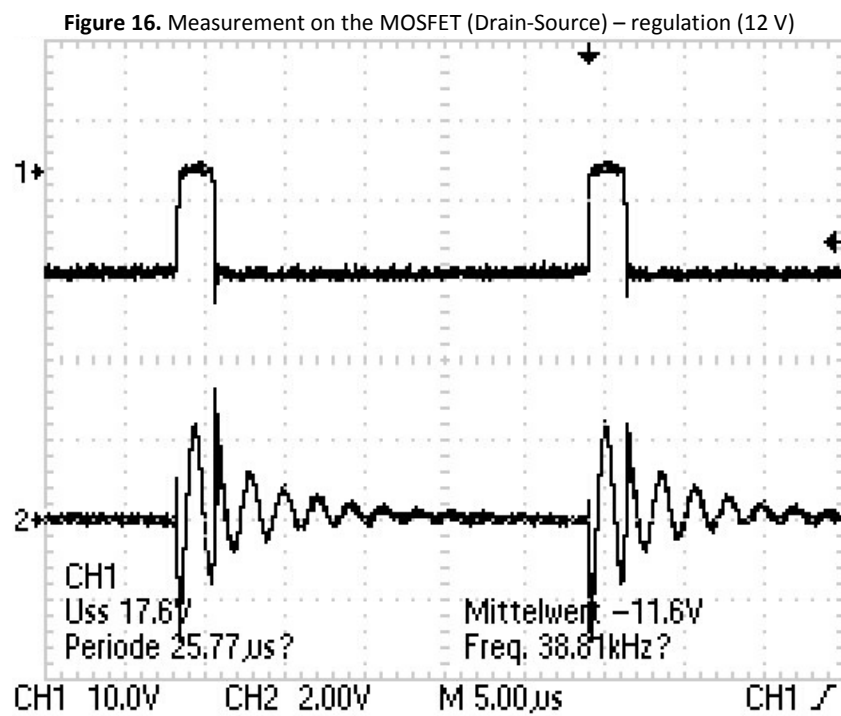


6.2.3 Diode

Ch1: $u_D(t)$

Ch2: $i_D(t)$

Figure 17. Measurement on the diode – regulation (12 V)

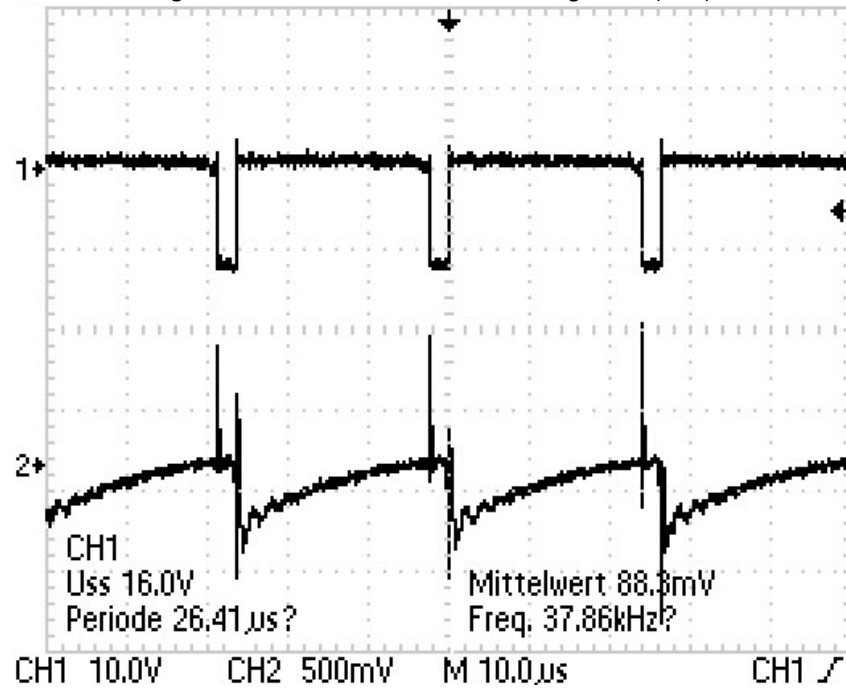


6.2.4 C_5

Ch1: $\Delta u_{C5}(t)$

Ch2: $i_{C5}(t)$

Figure 18. Measurement on C5 - regulation (12 V)

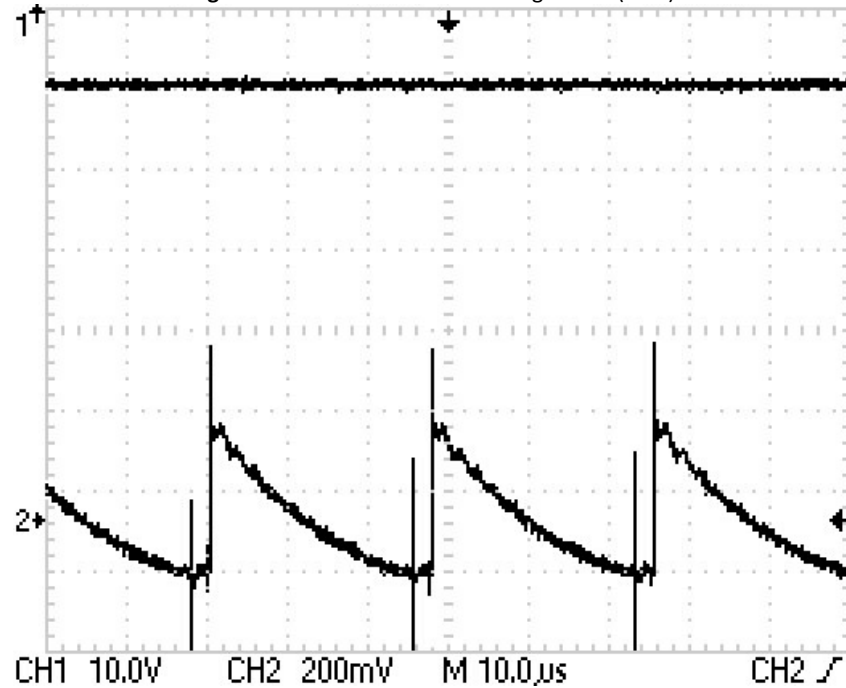


6.3 Measurement results at 18 V (maximum output voltage)

6.3.1 Coil

Ch1: $u_L(t)$

Ch2: $i_L(t)$

Figure 19. Measurement on the Coil - regulation (18 V)

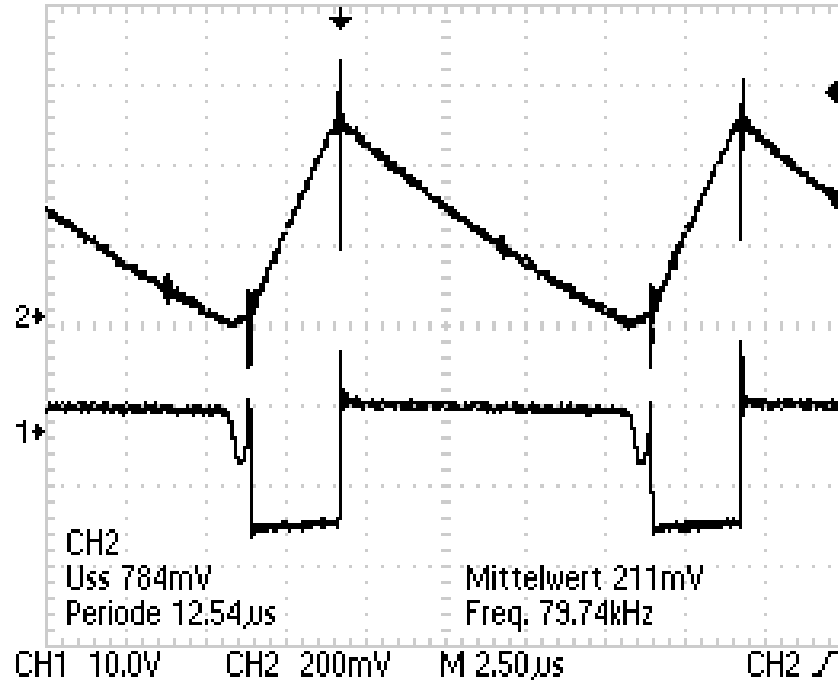


6.3.2 MOSFET (Drain-Source)

Ch1: $u_{DS}(t)$

Ch2: $i_{DS}(t)$


Figure 20. Measurement on the MOSFET (Drain-Source) - regulation (18 V)

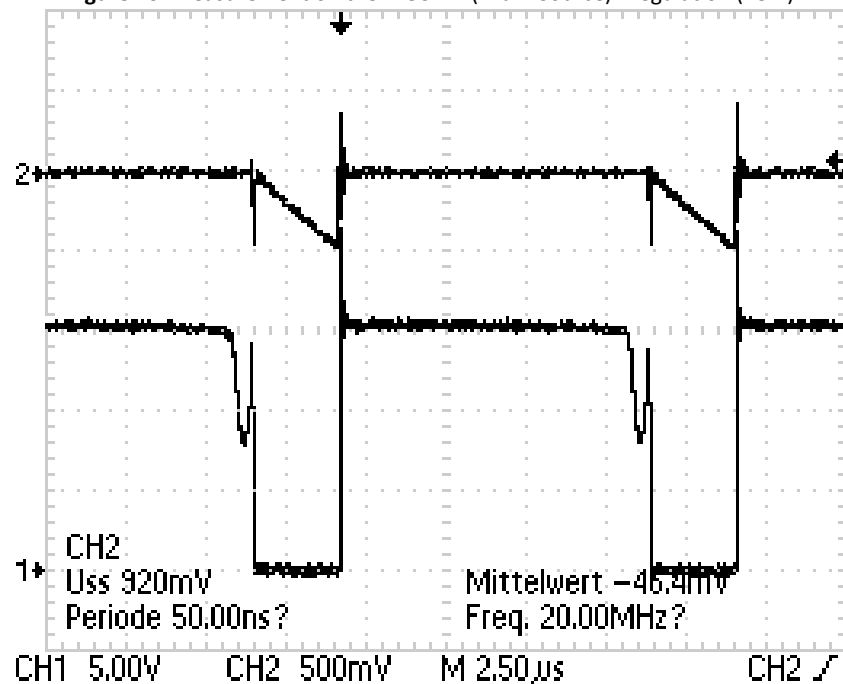

6.3.3 Diode

Ch1: $u_D(t)$


Ch2: $i_D(t)$

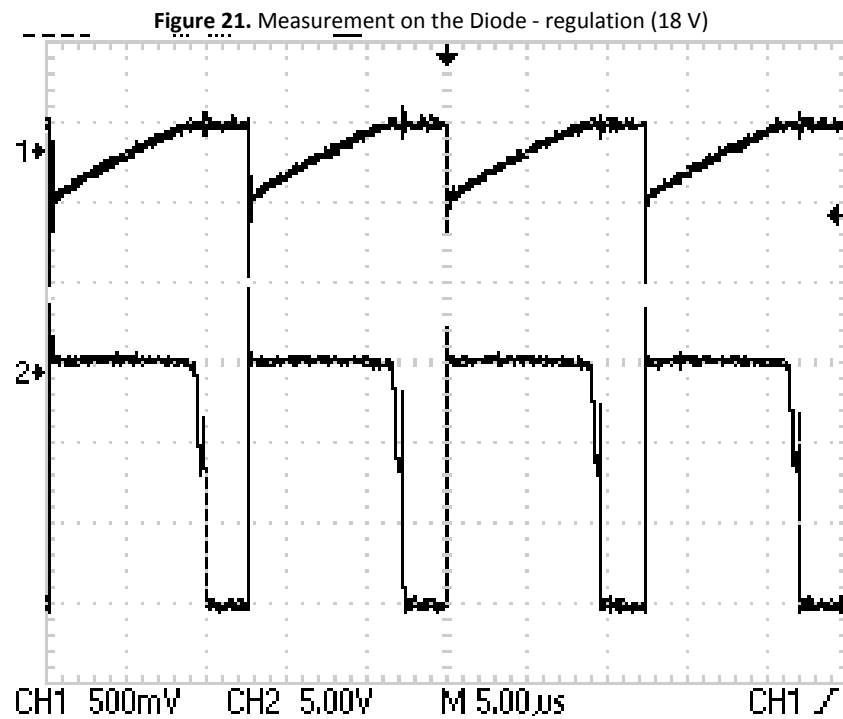

6.3.4 C_5

Ch1: $\Delta u_{C5}(t)$

Ch2: $i_{C5}(t)$

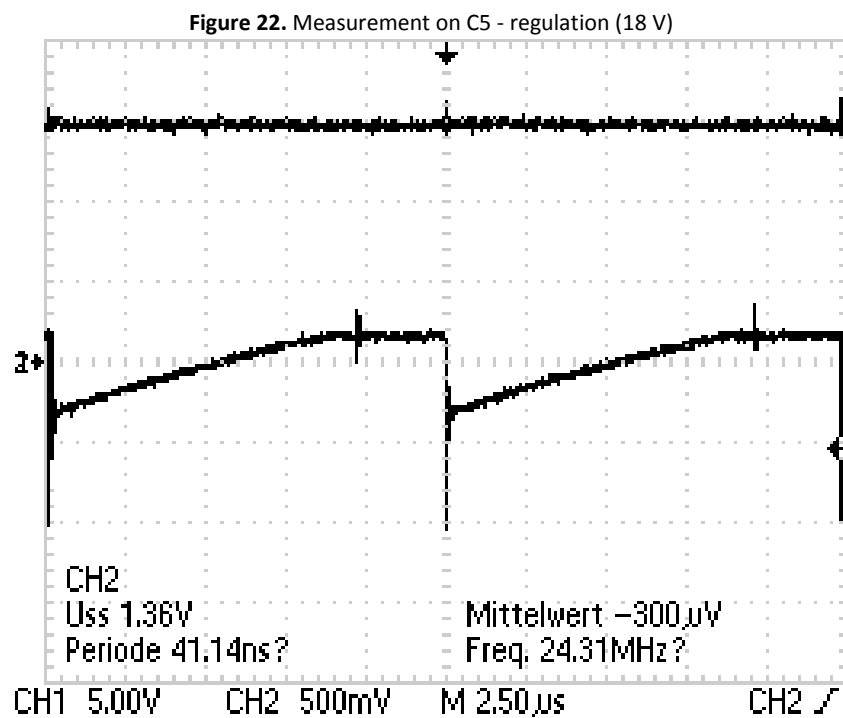

7 Step-Up Converter with regulation (12 V – 18 V) and Load Regulation

7.1 Measurement Setup

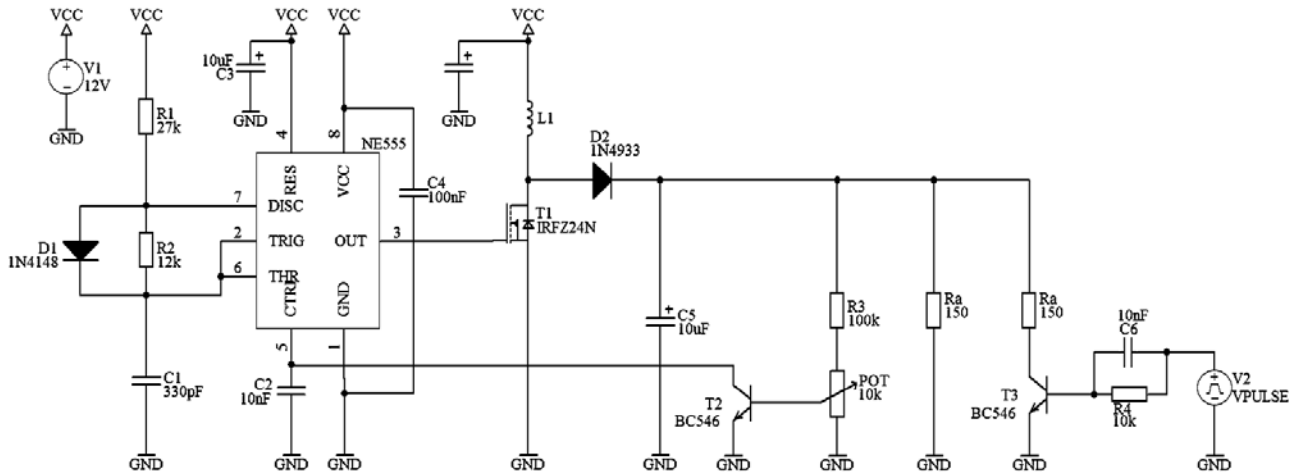


Figure 23. Complete circuit with regulation and load regulation

In this circuit the fluctuations of the output voltage are measured. These fluctuations are results of the temporal discharge of capacitor C5.

Exactly these fluctuations between the load regulation wave generator V2 and the output signal are measured.

7.2 Measurement Results

7.2.1 Input Signal

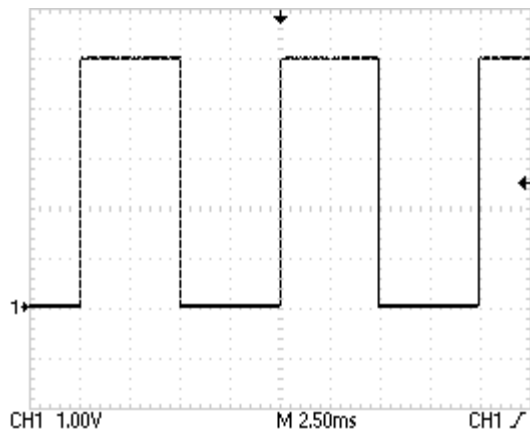


Figure 24. Input signal of the pulse generator

7.2.2

7.2.3 Output Signal

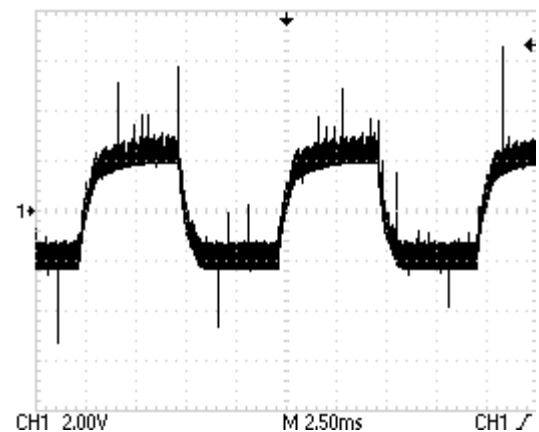


Figure 25. Output signal at the converter

8 Opto-isolator

8.1 Measurement Setup

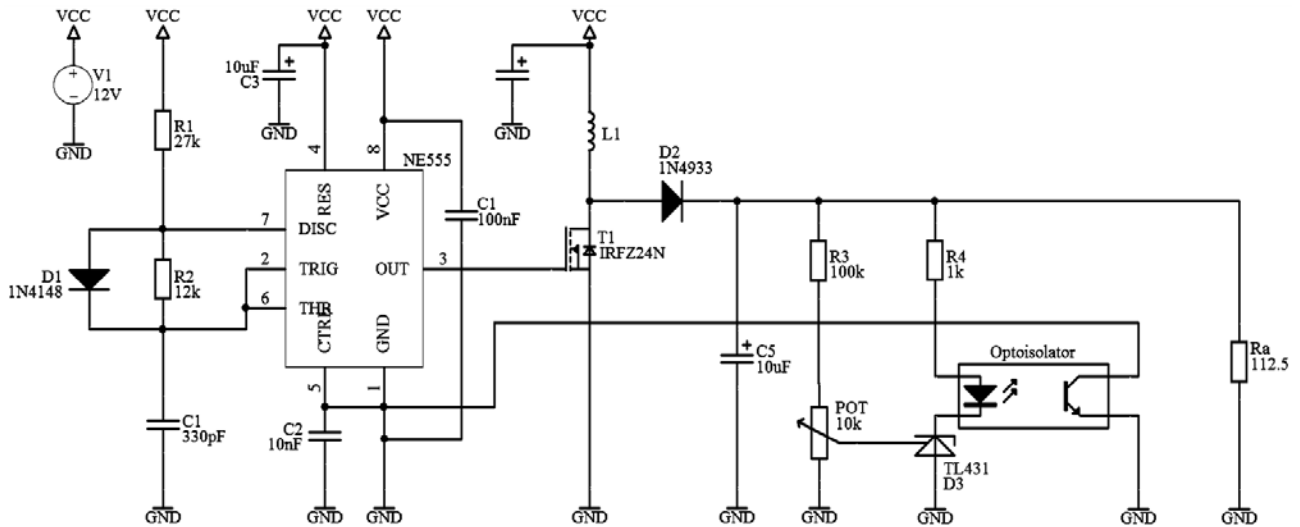


Figure 26. Complete circuit of the regulation with opto isolation

An opto isolator separates the output signal from the remaining part of the circuit. An opto isolator consists of a transmitter (IR-Diode) and a receiver (phototransistor). Both parts are integrated in the same chip.

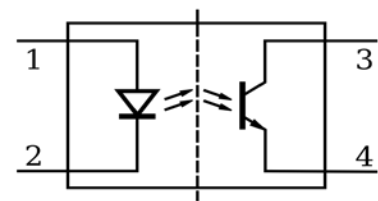


Figure 27. Internal circuit of an opto isolator

8.2 Measurement Results

8.2.1.1 Minimal output voltage

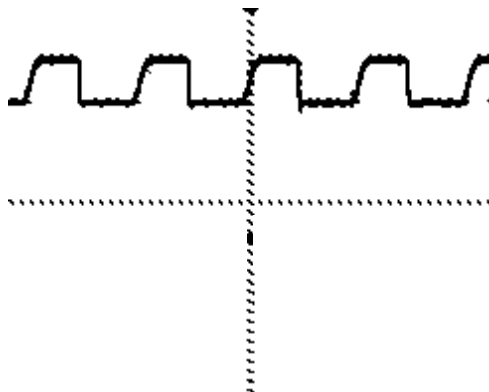


Figure 28. minimal output voltage – opto isolator

8.2.1.2 Maximal output voltage

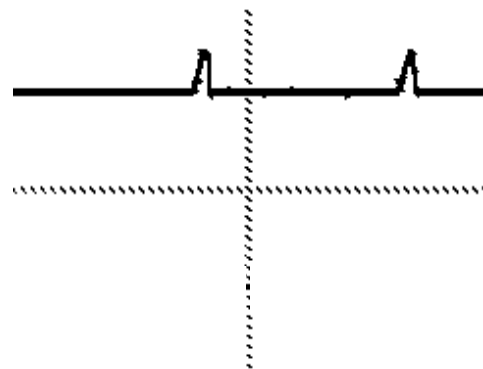


Figure 29. maximal output voltage – opto isolator

9 Register of Illustrations

Figure 1. Basic Concept of a Step-Up Converter	3
Figure 2. MOSFET as Switch.....	4
Figure 3. TO-220 case of the MOSFET	4
Figure 4. MOSFET circuit symbol	4
Figure 5. NE555 as an astable multivibrator	4
Figure 6. Complete circuit with fixed output voltage.....	7
Figure 7. Load resistance (R_A).....	7
Figure 8. Measurement Setup for oscilloscopes	7
Figure 9. Measurements on C1 and NE555 output - fixed output voltage	8
Figure 10. Measurements on the coil - fixed output voltage	8
Figure 11. Measurement on the MOSFET (Drain-Source) - fixed output voltage	9
Figure 12. Measurement on the diode - fixed output voltage.....	9
Figure 13. Measurement on C5 - fixed output voltage	10
Figure 14. Complete circuit with regulation.....	11
Figure 15. Measurement on the coil – regulation (12 V)	12
Figure 16. Measurement on the MOSFET (Drain-Source) – regulation (12 V).....	12
Figure 17. Measurement on the diode – regulation (12 V).....	13
Figure 18. Measurement on C5 - regulation (12 V).....	13
Figure 19. Measurement on the Coil - regulation (18 V).....	14
Figure 20. Measurement on the MOSFET (Drain-Source) - regulation (18 V).....	14
Figure 21. Measurement on the Diode - regulation (18 V)	15
Figure 22. Measurement on C5 - regulation (18 V).....	15
Figure 23. Complete circuit with regulation and load regulation	16
Figure 24. Input signal of the pulse generator	16
Figure 25. Output signal at the converter	16
Figure 26. Complete circuit of the regulation with opto isolation	17
Figure 27. Internal circuit of an opto isolator.....	17
Figure 28. minimal output voltage – opto isolator.....	17
Figure 29. maximal output voltage – opto isolator	17