

# PROTOCOL

to laboratory exercise

## *RC-Sine-Wave-Oscillator*

**HTL**  
St. Pölten

**EL**

Group / Class  <b>5 / 4BHELS</b>	Secretary  <b>HOFSTÄTTER A.</b>	Signature
Exercise- / Delivery date  <b>10. Feb. 2015</b> <b>17. Feb. 2015</b>	Employee  <b>BIEHL S.</b>	Signature
Teacher  <b>Tillich</b>	Employee	Signature
Grade	Employee	Signature

## *RC-Sine-Wave-Oscillator*

### Used Devices

Nr.	Device	Manufacturer	Type	Place Nr.
<b>1.</b>	Function Generator	HAMEG	HM8030-6	-
<b>2.</b>	Power Supply	Conrad	PS2403D	-
<b>3.</b>	Oscilloscope	Tektronix	TDS 1001B	-

### Used Programs

Nr.	Name	Version
<b>1.</b>	Altium Designer	13
<b>2.</b>	Micro-Cap	11

## 1 Table of Contents

---

<b>1</b>	<b>TABLE OF CONTENTS .....</b>	<b>2</b>
<b>2</b>	<b>TASKS.....</b>	<b>3</b>
<b>3</b>	<b>T-FILTER OSCILLATOR (NOTCH FILTER) .....</b>	<b>3</b>
<b>3.1</b>	<b>CALCULATIONS.....</b>	<b>3</b>
<b>3.2</b>	<b>MEASUREMENT CIRCUIT.....</b>	<b>3</b>
<b>3.3</b>	<b><math>V_{CC}</math> - DEPENDENCY .....</b>	<b>4</b>
<b>3.4</b>	<b>MEASUREMENT (TIME DOMAIN).....</b>	<b>4</b>
<b>3.5</b>	<b>MEASUREMENT (FFT).....</b>	<b>5</b>
<b>3.6</b>	<b>TOTAL HARMONIC DISTORTION.....</b>	<b>5</b>
<b>4</b>	<b>PHASE-SHIFTING-OSCILLATOR.....</b>	<b>6</b>
<b>4.1</b>	<b>MEASUREMENT CIRCUIT.....</b>	<b>6</b>
<b>4.2</b>	<b><math>V_{CC}</math> - DEPENDENCY .....</b>	<b>6</b>
<b>4.3</b>	<b>MEASUREMENT (TIME DOMAIN).....</b>	<b>6</b>
<b>4.4</b>	<b>MEASUREMENT (FFT).....</b>	<b>7</b>
<b>4.5</b>	<b>TOTAL HARMONIC DISTORTION.....</b>	<b>7</b>

## 2 Tasks

Task of this laboratory exercise was to build a several RC-Oscillator Circuit.

1. Calculation
2. Setup and Realisation
3. Measurement of the  $V_{cc}$ -Dependency
4. Measurement (Time domain and FFT)
5. Calculation of the Total Harmonic Distortion (THD)

The following RC-Oscillator circuits were built.

- T-Filter Oscillator (Notch filter)
- Phase-Shifting-Oscillator

All Oscillators were provided with an unsymmetrical power supply.

$$GND = 0 V$$

$$V_{cc} = 15 V$$

The cut off frequency for all following calculations and setups was  $f_G = 300 \text{ Hz}$ .

## 3 T-Filter Oscillator (Notch filter)


### 3.1 Calculations

Based on the given cut off frequency of 300 Hz the values for R and C were calculated. It was assumed that the capacitor has a value of 33nF.

$$C = 33 \text{ nF}$$

$$f_g = \frac{1}{2 * \pi * R * C} \rightarrow R = \frac{1}{f_g * 2 * \pi * C} = \frac{1}{300 \text{ Hz} * 2 * \pi * 33 \text{ nF}} = 16 \text{ k}\Omega \rightarrow R = 15 \text{ k}\Omega$$

### 3.2 Measurement Circuit

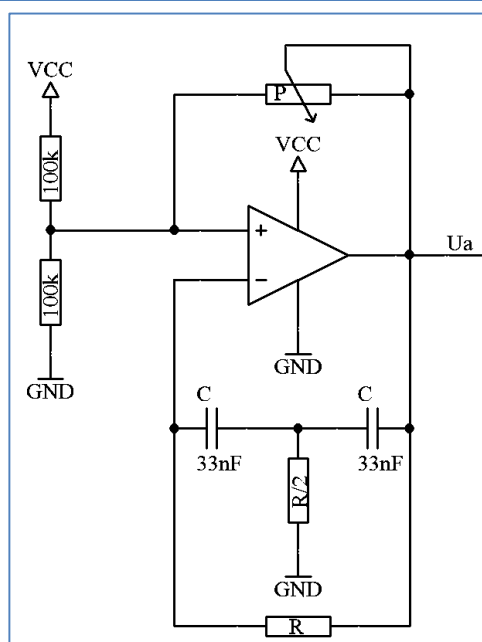


$$R = 15 \text{ k}\Omega$$

$$\frac{R}{2} = 7.2 \text{ k}\Omega$$


$$P = 100 \text{ k}\Omega$$

$$C = 33 \text{ nF}$$


### 3.3 $V_{CC}$ - Dependency

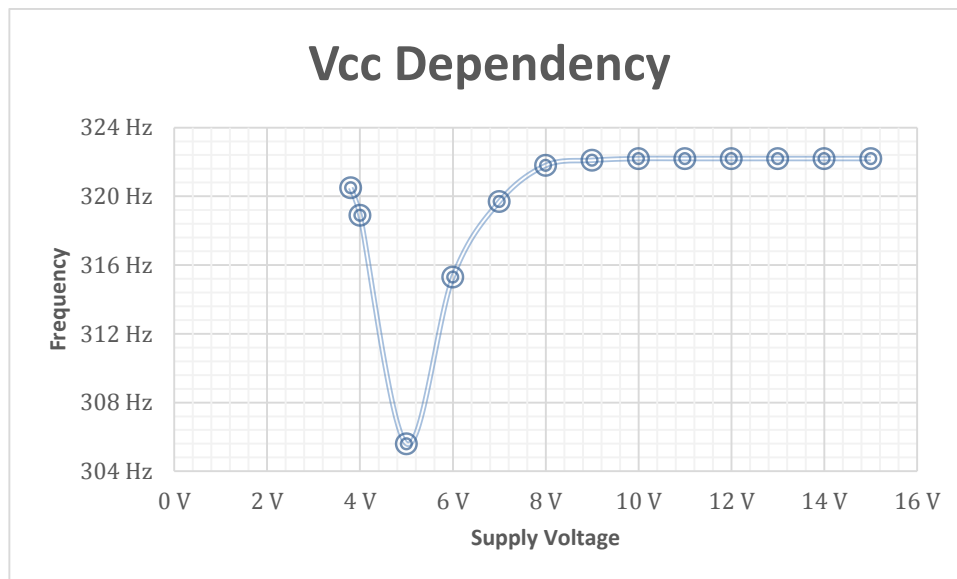

### 3.4 Measurement (Time Domain)

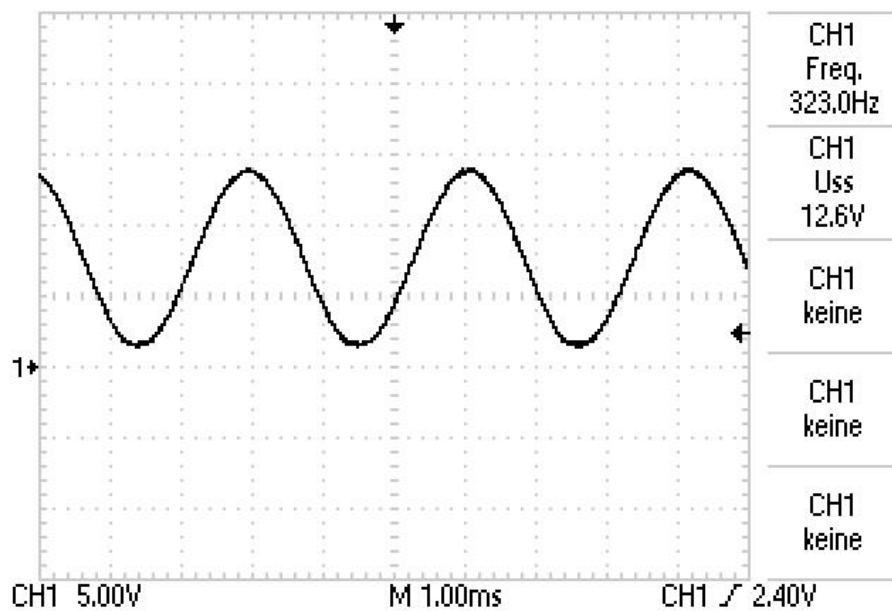

### 3.5 Measurement (FFT)

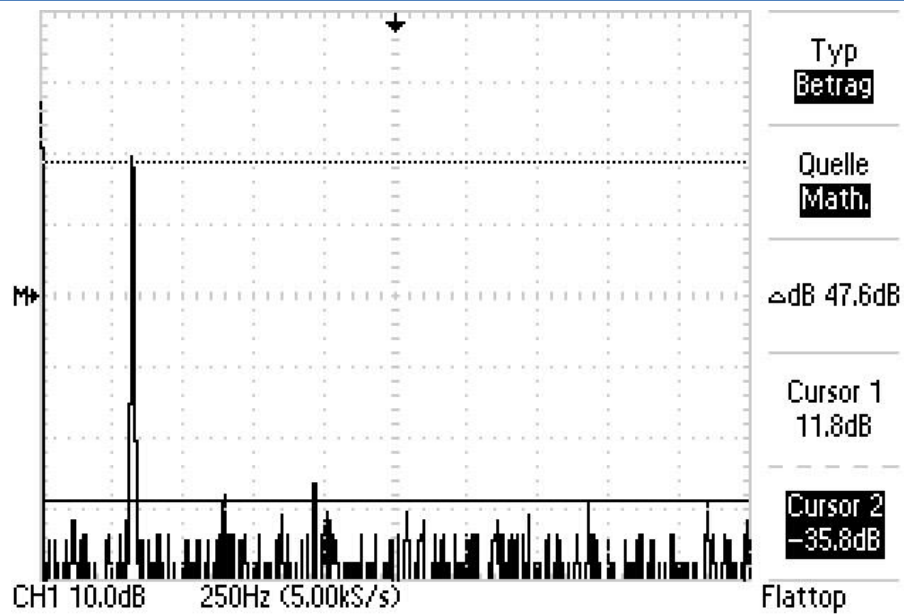


### 3.6 Total Harmonic Distortion

Based on above measurement (FFT) the difference between the cursors was taken for the following calculations. ( $\Delta$ Cursor = 47,6 dB)

$$k = 10^{\frac{47,6 \text{ dB}}{20}} \cong 240 \rightarrow \frac{1}{240} = 4,16 \text{ mV} \rightarrow 14,16 \text{ mV} * \sqrt{2} = 5,88 \text{ mV} = 5,8 \%$$

## 4 Phase-Shifting-Oscillator

### 4.1 Measurement Circuit

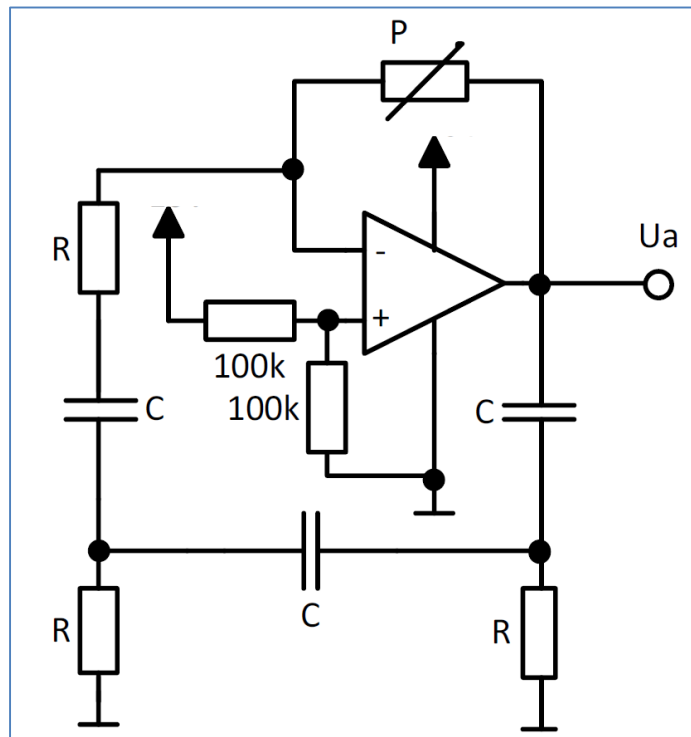

$$R = 15 \text{ k}\Omega$$

$$\frac{R}{2} = 7.2 \text{ k}\Omega$$


$$P = 1 \text{ M}\Omega$$

$$C = 33 \text{ nF}$$


### 4.2 $V_{cc}$ - Dependency

The oscillator frequency has not changed with a modified supply voltage.

### 4.3 Measurement (Time Domain)

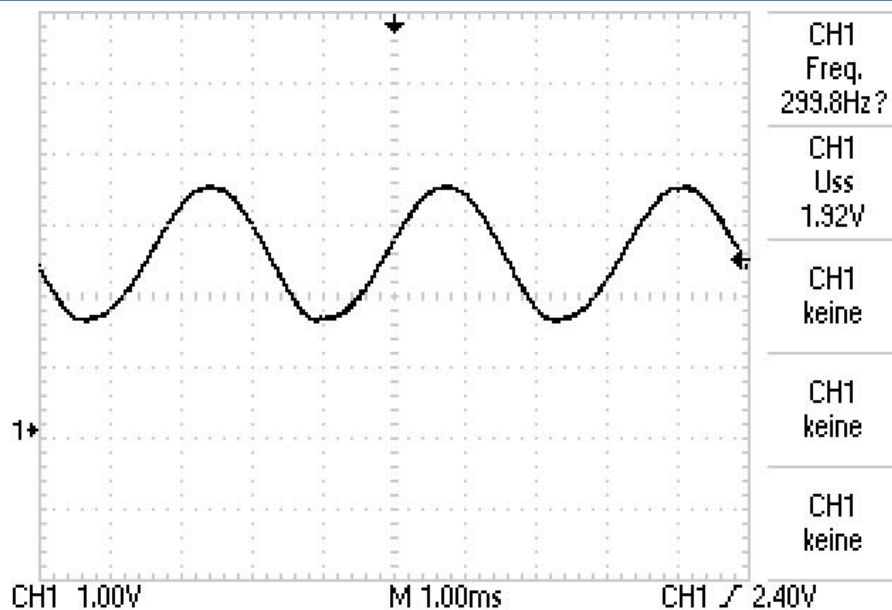

#### 4.4 Measurement (FFT)

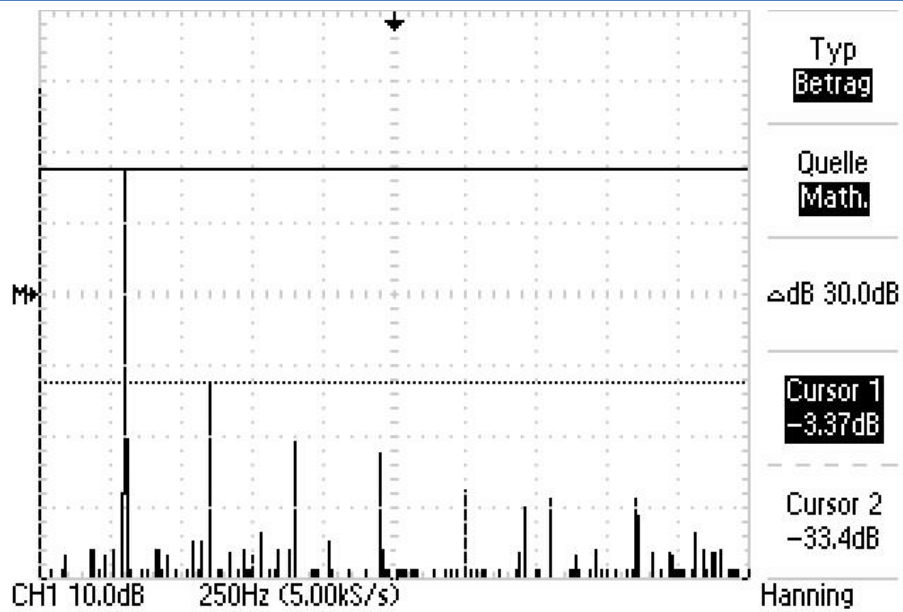

#### 4.5 Total Harmonic Distortion

Based on above measurement (FFT) the difference between the cursors was taken for the following calculations.

##### *First Harmonic*

$$\Delta \text{Cursor 1} = 30 \text{ dB}$$
$$k = 4.5 \%$$

##### *Second Harmonic*

$$\Delta \text{Cursor 2} = 37 \text{ dB}$$
$$k = 1.9 \%$$

##### *Third Harmonic*

$$\Delta \text{Cursor 3} = 40 \text{ dB}$$
$$k = 1.4 \%$$