

# PROTOCOL

for lab-exercise

## LC-Oscillator

**HTL**  
St. Pölten

**EL**

Group / Class <b>5 / 4AHELS</b>	Script writer <b>Thomas ASCH</b>	Signature
Date of Exercise / Hand-in Date <b>1.4.2014</b> <b>8.4.2014</b>	Team member <b>Andreas BÖHM</b>	Signature
Teacher <b>TILL</b>	Team member <b>Peter Neunteufel</b>	Signature
Grade	Team member	Signature

### SUMMARY (or DEVICE UNDER TEST)

LC-Oscillator

### USED DEVICES

Number	Device	Company	Type	Inventory Number
1	Laboratory Power Supply	Tecstar	PS 2403D	EL-TFTKL 0057/02
2	Oszilloskop	Tektronics	TDS1001B	540-04/2007/5/16
3				

Stored on el-lab file Server: \_\_\_\_\_

## LC-Oscillator

### Task 1:

Design an LC oscillator using a collector-ground circuit. The oscillator should have a frequency of approximately 900 kHz and a coil with 22μH. Build this circuit on the breadboard. Measure the voltage course and the FFT of the output voltage  $U_a$  with the oscilloscope.

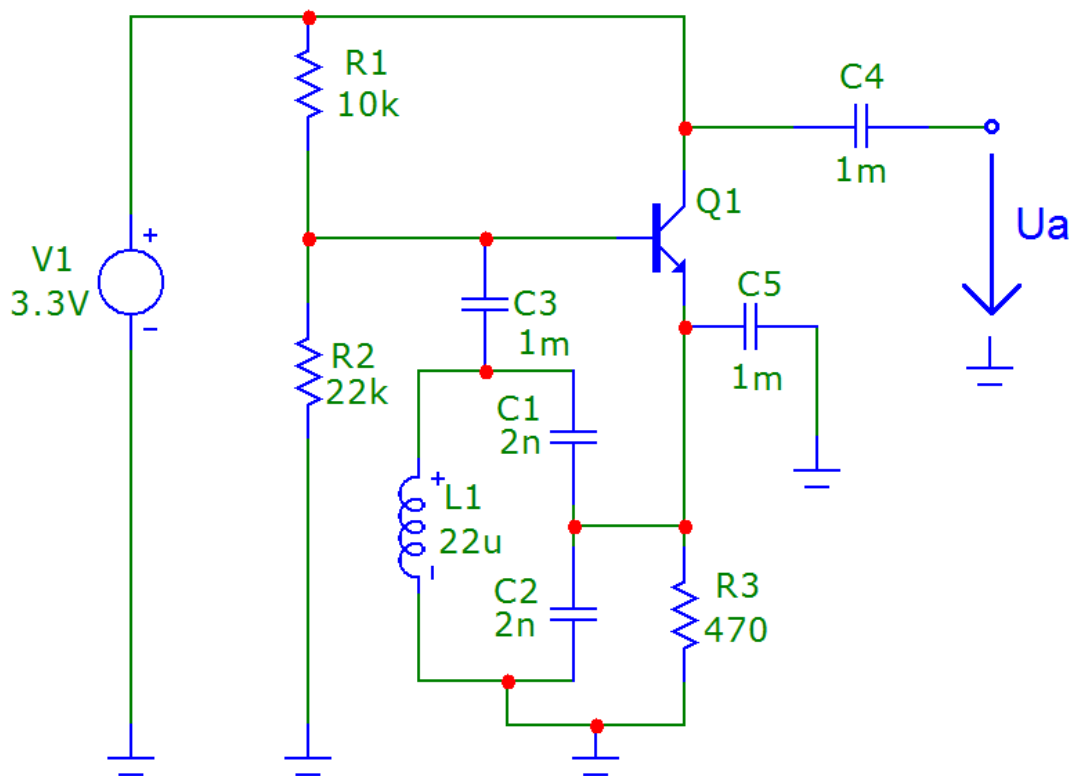


Fig. 1: Collector-ground circuit

### Calculations:

$$f_o = \frac{1}{2\pi \cdot \sqrt{L \cdot C_{ges}}} \quad / \cdot \sqrt{L} \quad / \cdot 2\pi$$

$$f_o \cdot 2\pi \cdot \sqrt{L} = \frac{1}{\sqrt{C_{ges}}} \quad /^2$$

$$\left( \frac{1}{2\pi \cdot f_o \cdot \sqrt{L}} \right)^2 = C_{ges}$$

$$C_{ges} = \left( \frac{1}{2\pi \cdot 900k \cdot \sqrt{22\mu}} \right)^2 = 2nF$$

## LC-Oscillator

$$C_{ges} = \frac{C1 * C2}{C1 + C2} \quad \Rightarrow \quad C1, C2 = 2nF$$

$$U_{R2} = U_o * \frac{R1}{R1 + R2}$$

$$U_{R2} = 3,3V * \frac{10k}{10k + 22k} = 2,27V$$

### Measurements:

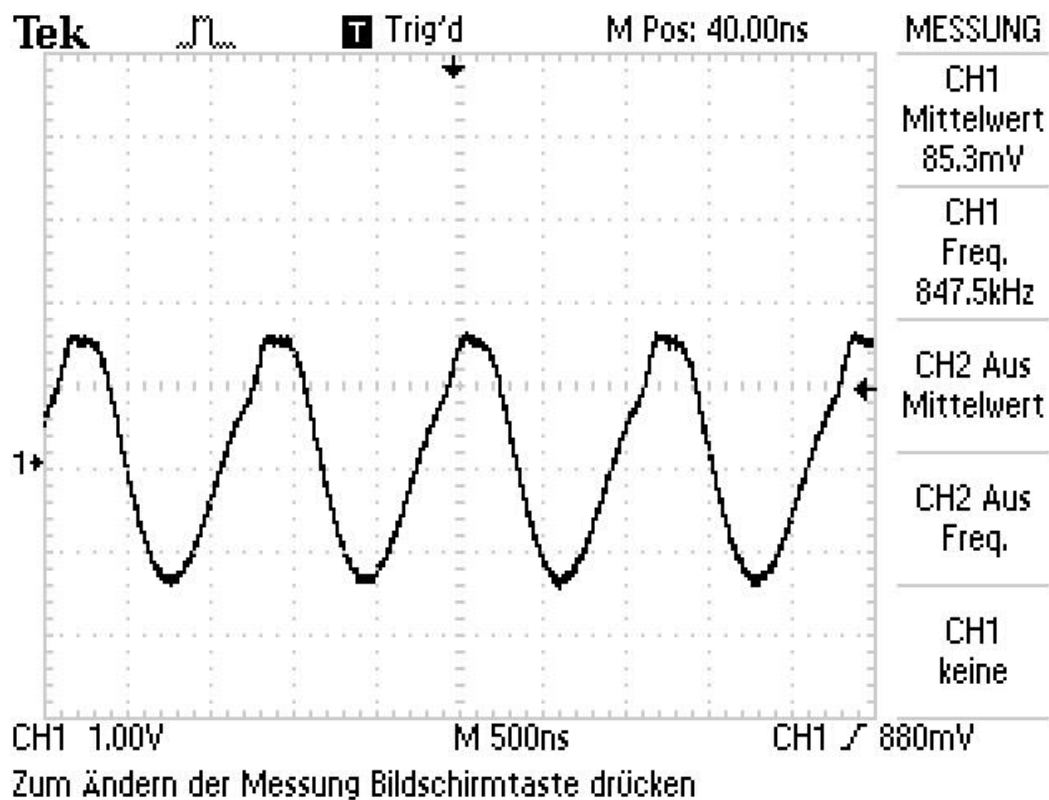


Fig. 2: Voltage course of the output voltage  $U_a$

## LC-Oscillator

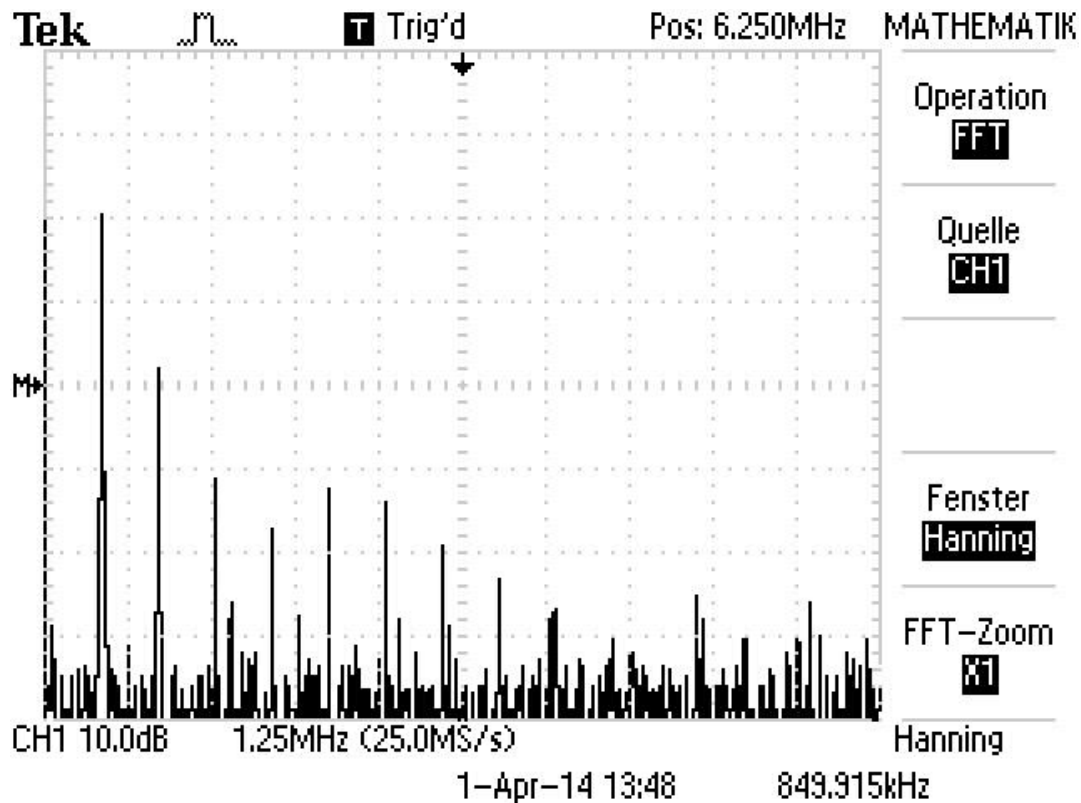


Fig. 3: FFT of the output voltage  $U_a$

### Calculation of the distortion factor:

U1/dBV	U1/V	U2/dBV	U2/V	U3/dBV	U3/V	U4/dBV	U4/V
20	10	2	1,26	-11	0,28	-17	0,14

$$K = \sqrt{\frac{1,26^2 + 0,28^2 + 0,14^2}{10^2 + 1,26^2 + 0,28^2 + 0,14^2}} = 0,129 \Rightarrow 12,9\%$$

### Comment:

After the 4th harmonic the FFT is uninteresting. In Figure 2 we see that the sine is not very nice. There were no problems in the construction and in the measurement.

## LC-Oscillator

### Task 2:

Design an LC oscillator using an emitter circuit. The oscillator should have a frequency of approximately 900 kHz and a coil with 22μH. Build this circuit on the breadboard. Measure the voltage course and the FFT of the output voltage  $U_a$  with the oscilloscope.

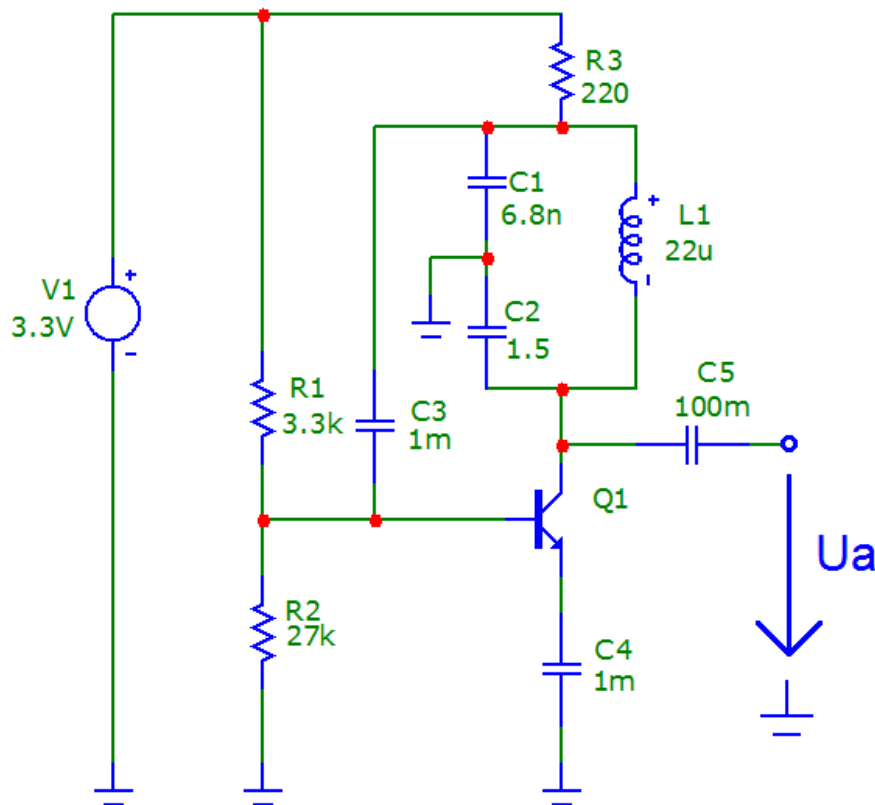


Fig. 4: Emitter circuit

### Calculations:

C1 should 5- 10-times be as large as C2

$$\Rightarrow C1 = 6,8n$$

$$\Rightarrow C2 = 1,5n$$

$$R3 = 0,65V / 3mA = 220\Omega$$

$$R4 = 2V / 3mA = 666,67\Omega \quad \Rightarrow R4 = 680\Omega$$

## LC-Oscillator

### Measurements:

Our variant with the resistor R3:

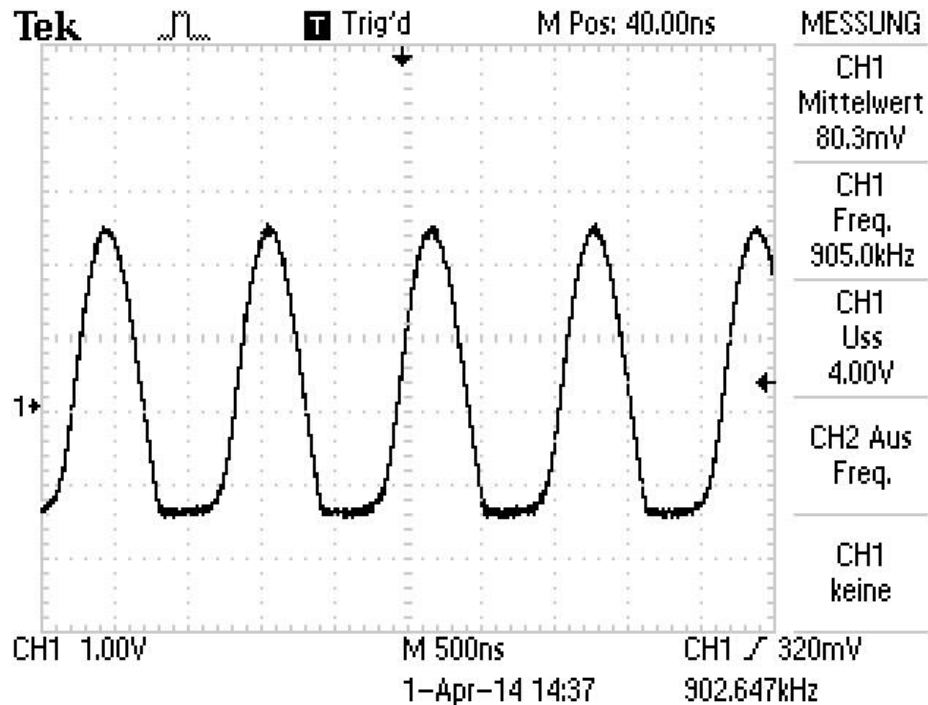


Fig. 5: Voltage course of the output voltage Ua

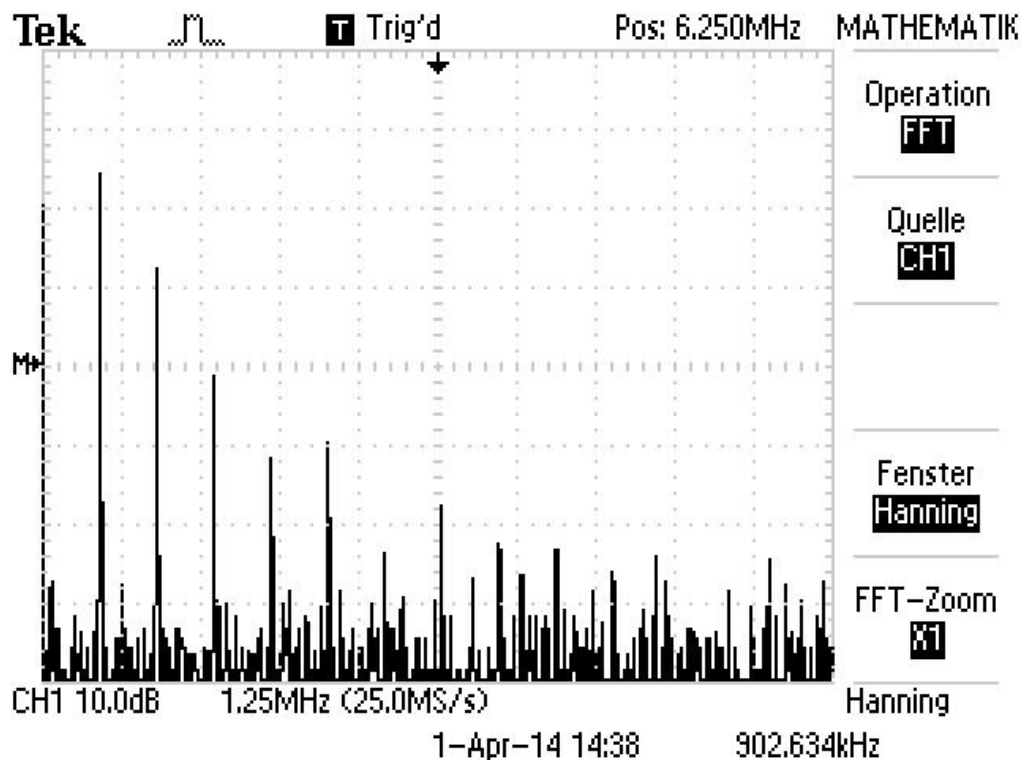


Fig. 6: FFT of the output voltage Ua

## LC-Oscillator

### Calculation of the distortion factor:

U1/dBV	U1/V	U2/dBV	U2/V	U3/dBV	U3/V	U4/dBV	U4/V
25	17,78	12	3,98	-1	0,89	-11	0,28

$$K = \sqrt{\frac{3,98^2 + 0,89^2 + 0,28^2}{17,78^2 + 3,98^2 + 0,89^2 + 0,28^2}} = 0,224 \Rightarrow 22,4\%$$

Variant of Prof. Tillich without the resistor R3:

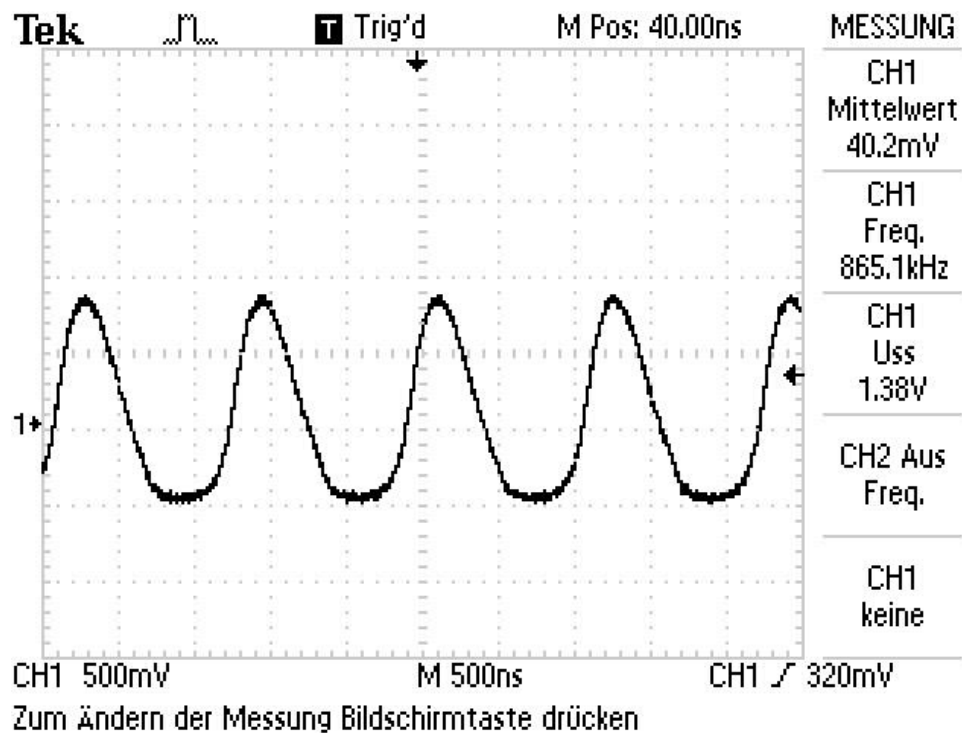


Fig. 7: Voltage course of the output voltage Ua

## LC-Oscillator

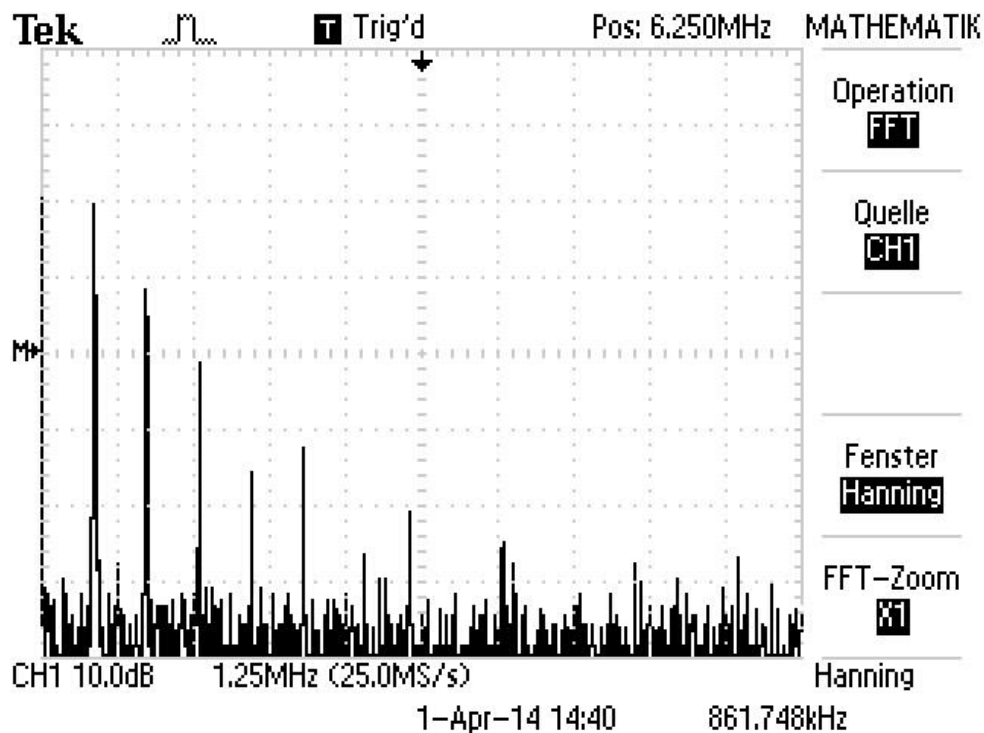


Fig. 8: FFT of the output voltage  $U_a$

### Calculation of the distortion factor:

U1/dBV	U1/V	U2/dBV	U2/V	U3/dBV	U3/V	U4/dBV	U4/V
20	10	9	2,82	-1	0,89	-15	0,18

$$K = \sqrt{\frac{2,82^2 + 0,89^2 + 0,18^2}{10^2 + 2,82^2 + 0,89^2 + 0,18^2}} = 0,284 \Rightarrow 28,4\%$$

### Comment:

In Figure 5 it can be seen that our variant is better with the resistor R3 because the sine look better. After the 4<sup>th</sup> harmonic the FFT is uninteresting. There were no problems in the construction and in the measurement.



## LC-Oscillator

### Task 3:

Design a Low-Cost oscillator. The oscillator should have a frequency of approximately 900 kHz and a coil with  $22\mu\text{H}$ . Build this circuit on the breadboard. Measure the voltage course and the FFT of the output voltage  $U_a$  with the oscilloscope.

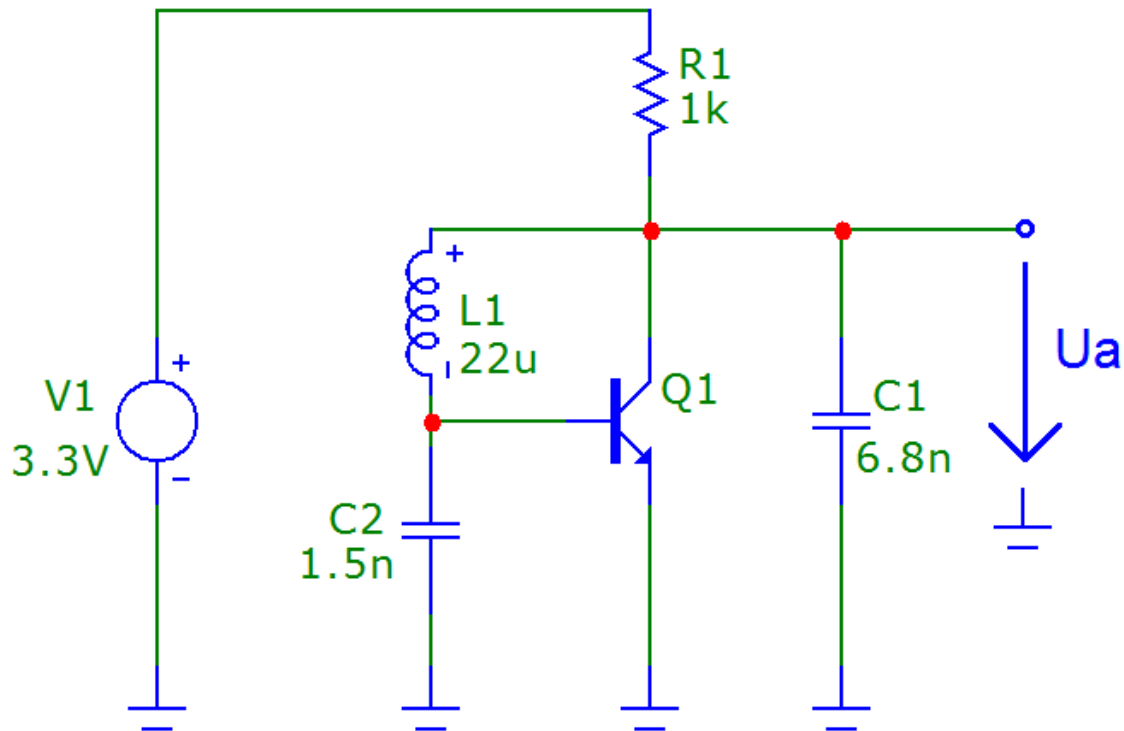


Fig. 9: Low-Cost-Oscillator

### Calculations:

C1 should 5-10-times be as large as C2

$$\Rightarrow C1 = 6,8\text{n}$$

$$\Rightarrow C2 = 1,5\text{n}$$

## LC-Oscillator

### Measurements:

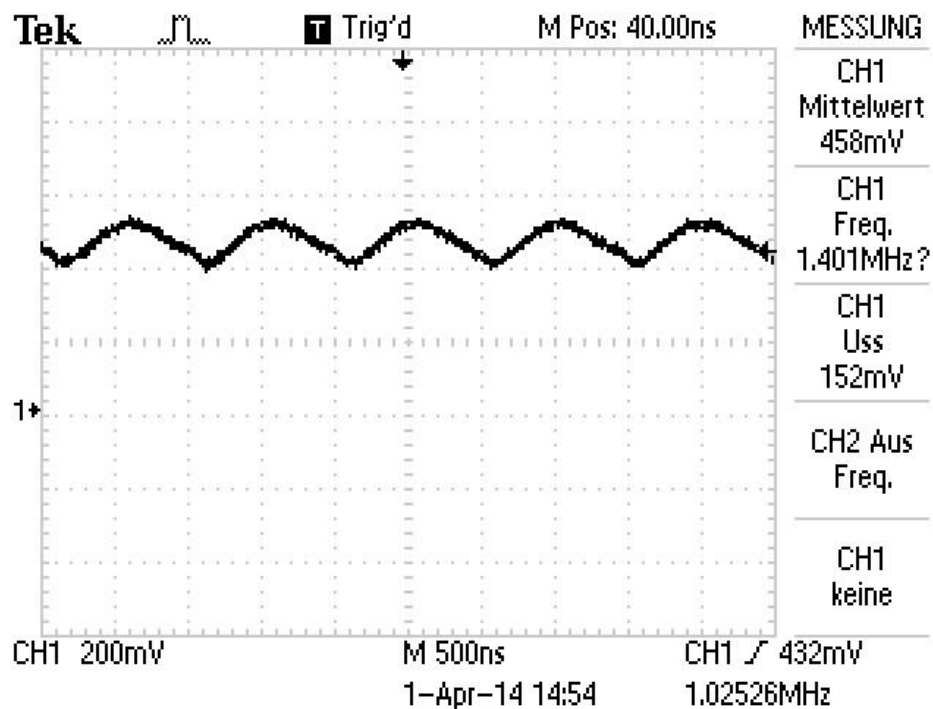


Fig. 10: Voltage course of the output voltage  $U_a$  at a supply voltage of 0,7V

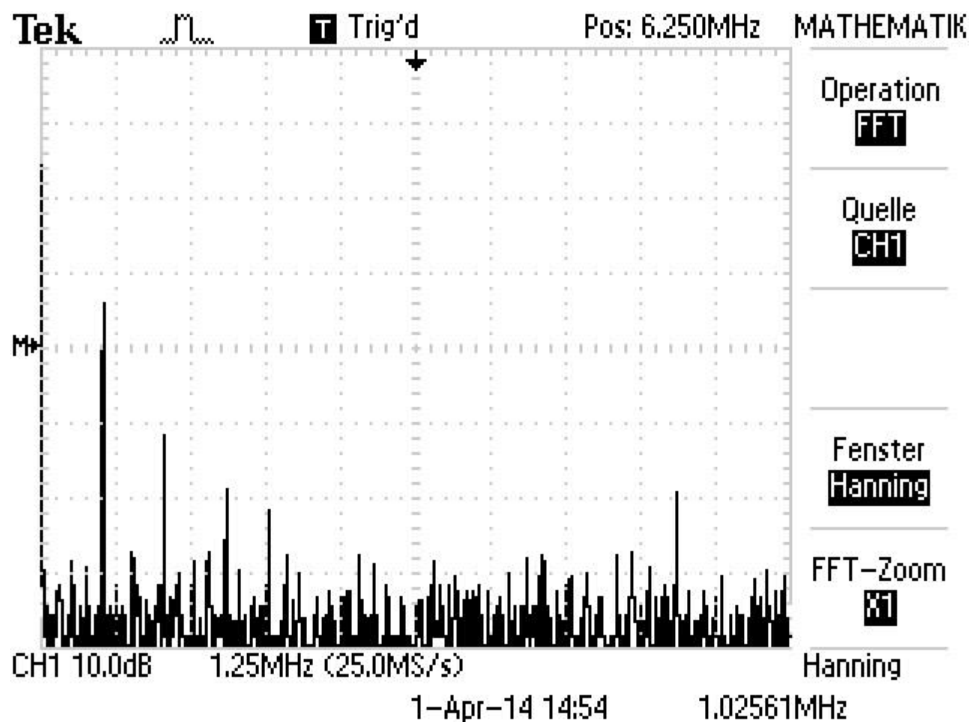


Fig. 11: FFT of the output voltage  $U_a$  at a supply voltage of 0,7V

## LC-Oscillator

### Calculation of the distortion factor:

U1/dBV	U1/V	U2/dBV	U2/V	U3/dBV	U3/V	U4/dBV	U4/V
7	2,24	-10	0,316	-18	0,126	-21	0,089

$$K = \sqrt{\frac{0,316^2 + 0,126^2 + 0,089^2}{2,24^2 + 0,316^2 + 0,126^2 + 0,089^2}} = 0,157 \Rightarrow 15,7\%$$

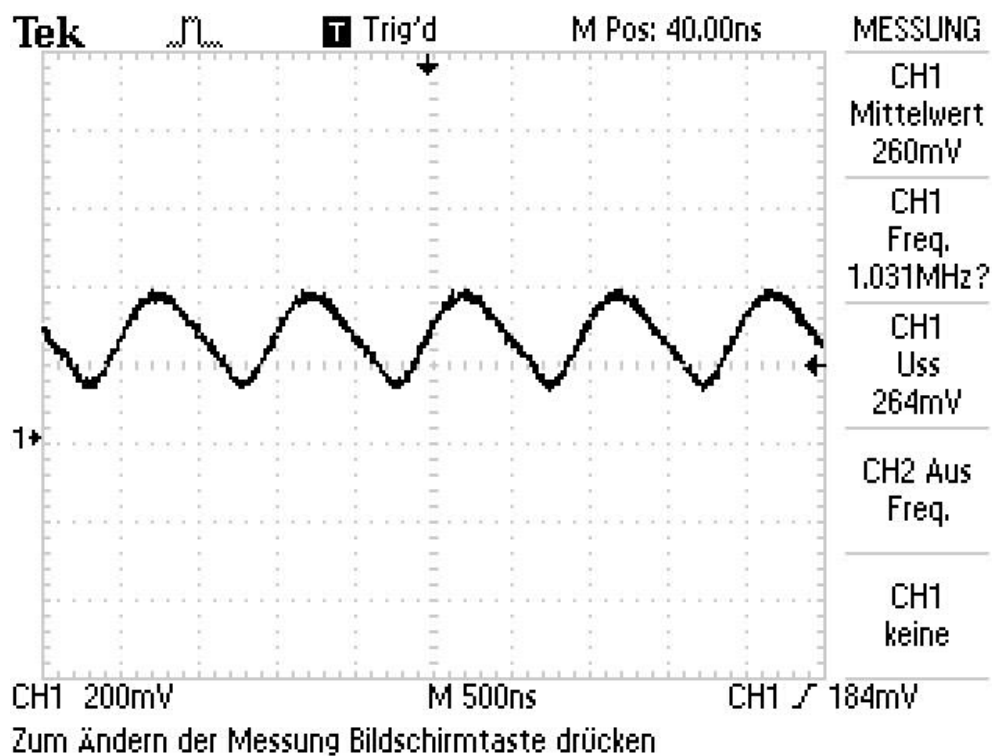


Fig. 12: Voltage course of the output voltage  $U_a$   
at a supply voltage of 1V

## LC-Oscillator

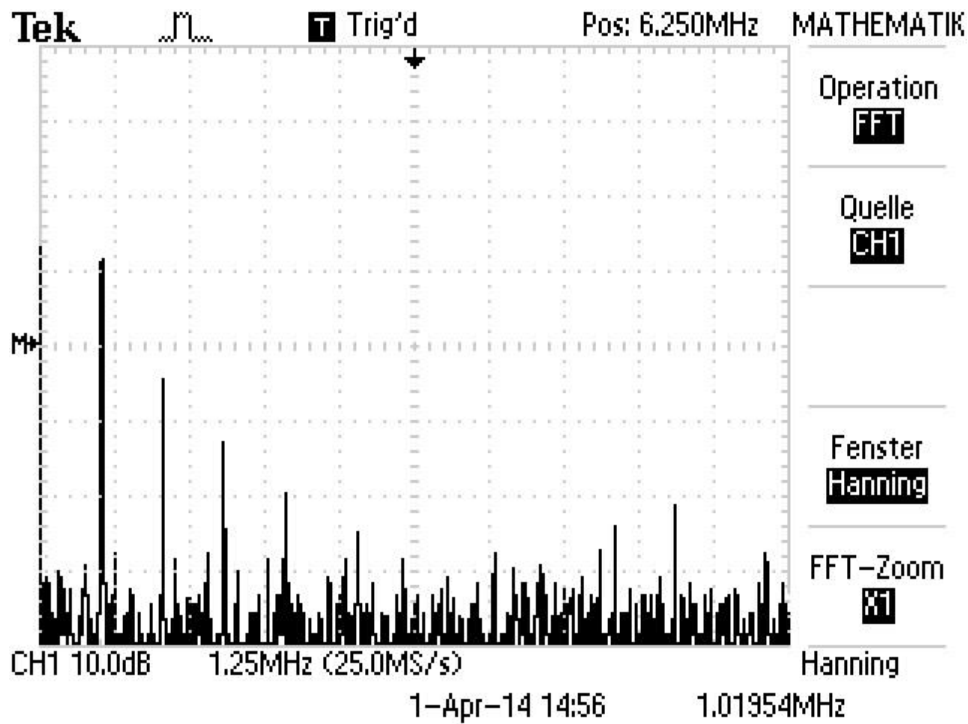


Fig. 13: FFT of the output voltage  $U_a$   
at a supply voltage of 1V

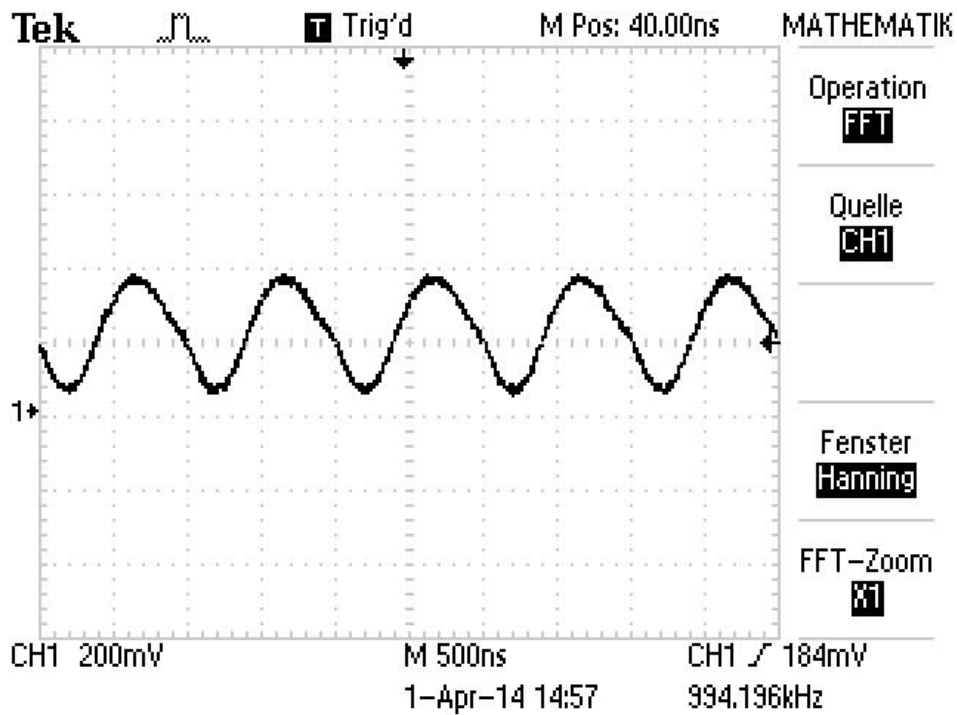


Fig. 14: Voltage course of the output voltage  $U_a$   
at a supply voltage of 1,5V

## LC-Oscillator

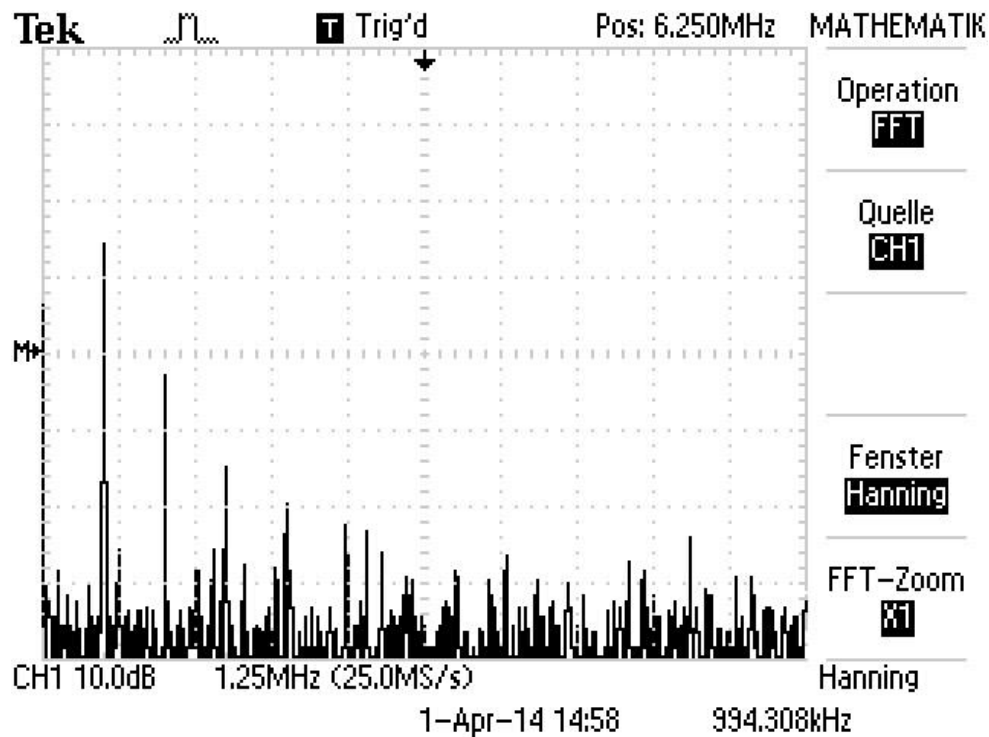


Fig. 15: FFT of the output voltage  $U_a$  at a supply voltage of 1,5V

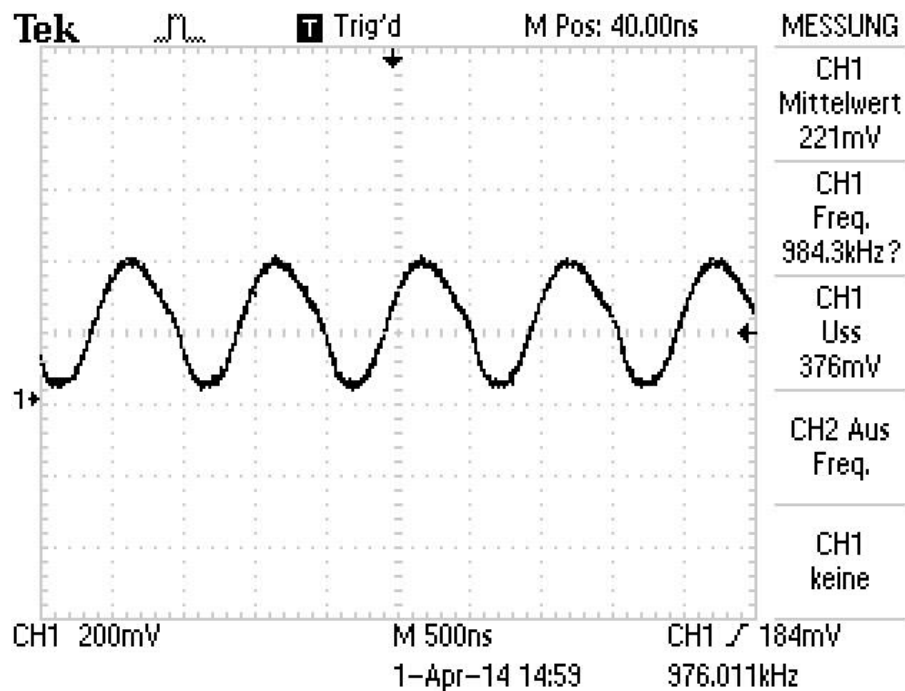


Fig. 16: Voltage course of the output voltage  $U_a$  at a supply voltage of 2V

## LC-Oscillator

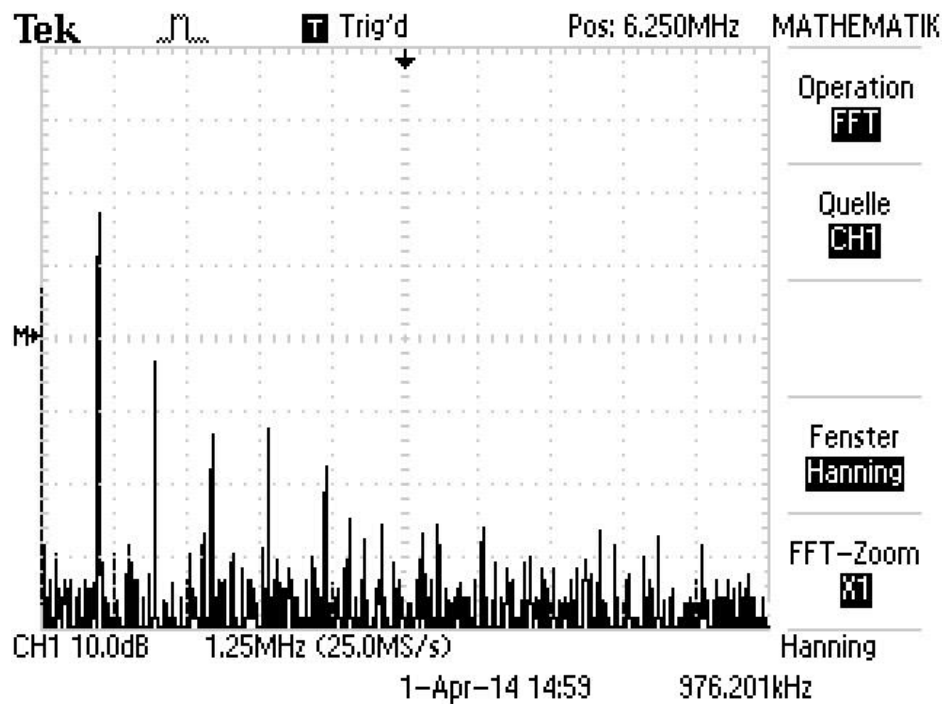


Fig. 17: FFT of the output voltage  $U_a$  at a supply voltage of 2V

### Calculation of the distortion factor:

U1/dBV	U1/V	U2/dBV	U2/V	U3/dBV	U3/V	U4/dBV	U4/V
18	7,94	-2	0,794	-13	0,224	-13	0,224

$$K = \sqrt{\frac{0,794^2 + 0,224^2 + 0,224^2}{7,94^2 + 0,794^2 + 0,224^2 + 0,224^2}} = 0,106 \Rightarrow 10,6\%$$

## LC-Oscillator

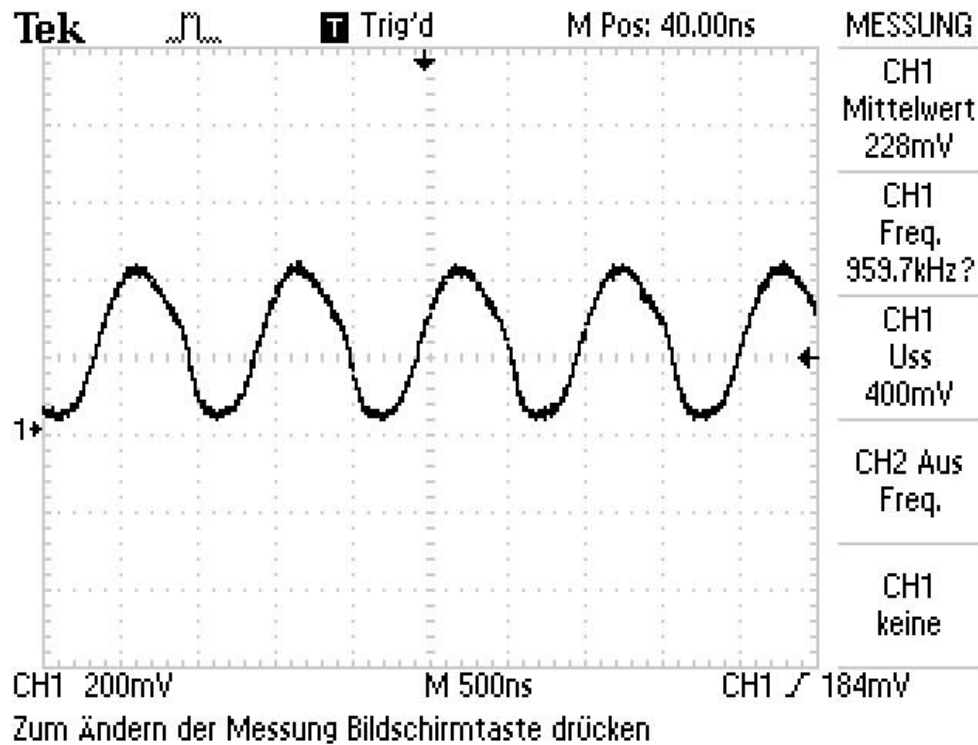


Fig. 18: Voltage course of the output voltage  $U_a$  at a supply voltage of 2,5V

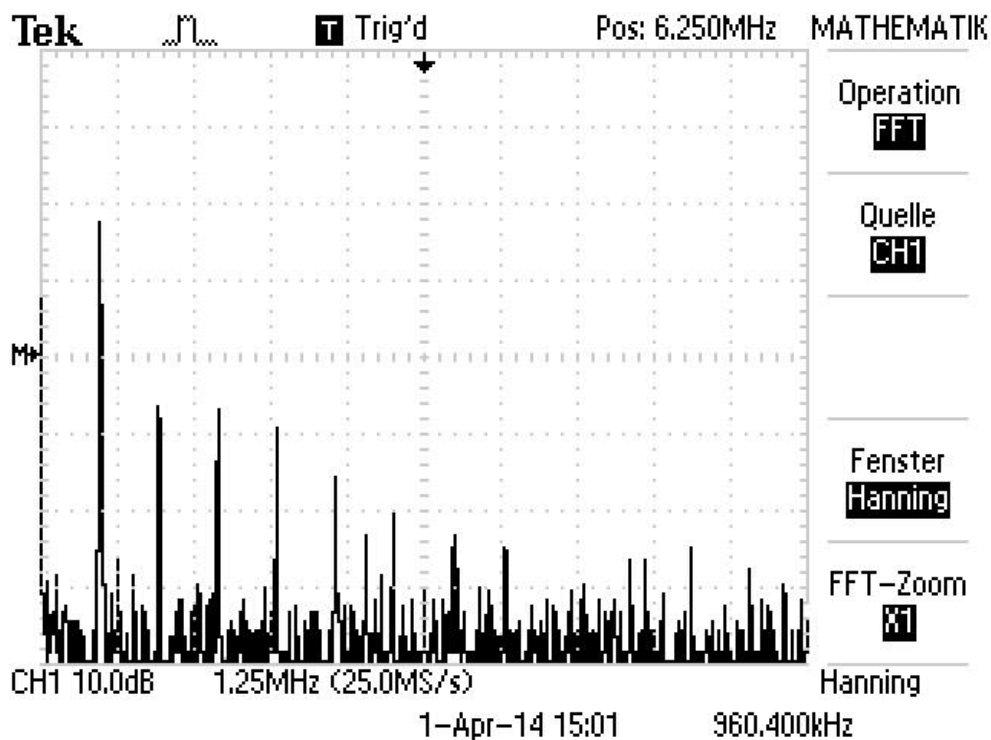


Fig. 19: FFT of the output voltage  $U_a$  at a supply voltage of 2,5V

## LC-Oscillator

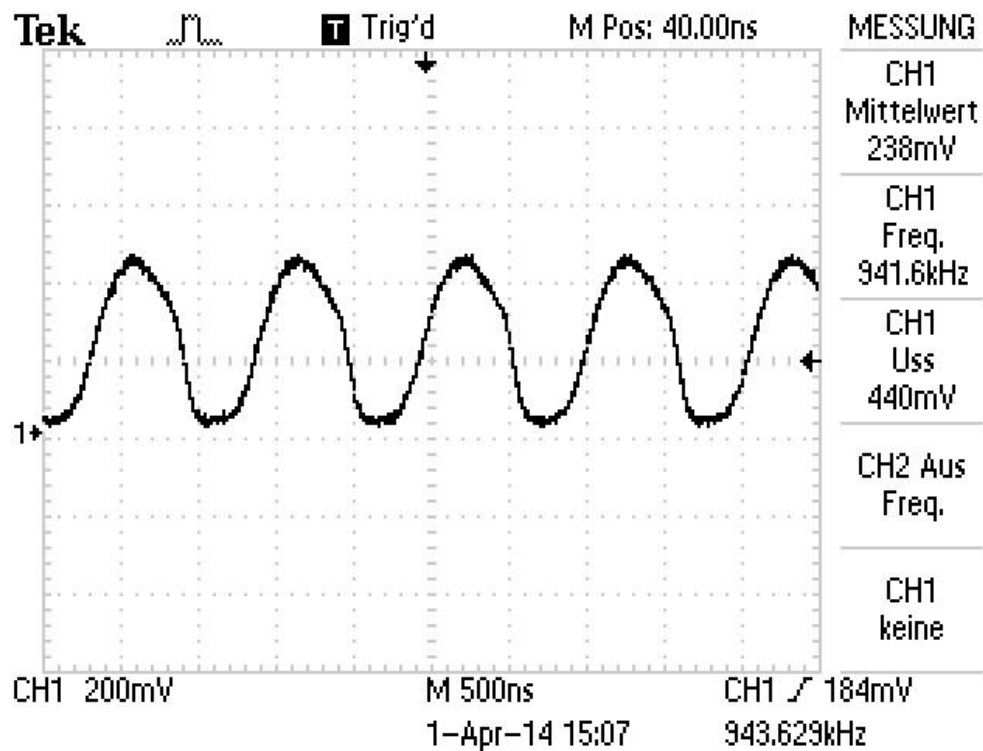


Fig. 20: Voltage course of the output voltage  $U_a$  at a supply voltage of 3V

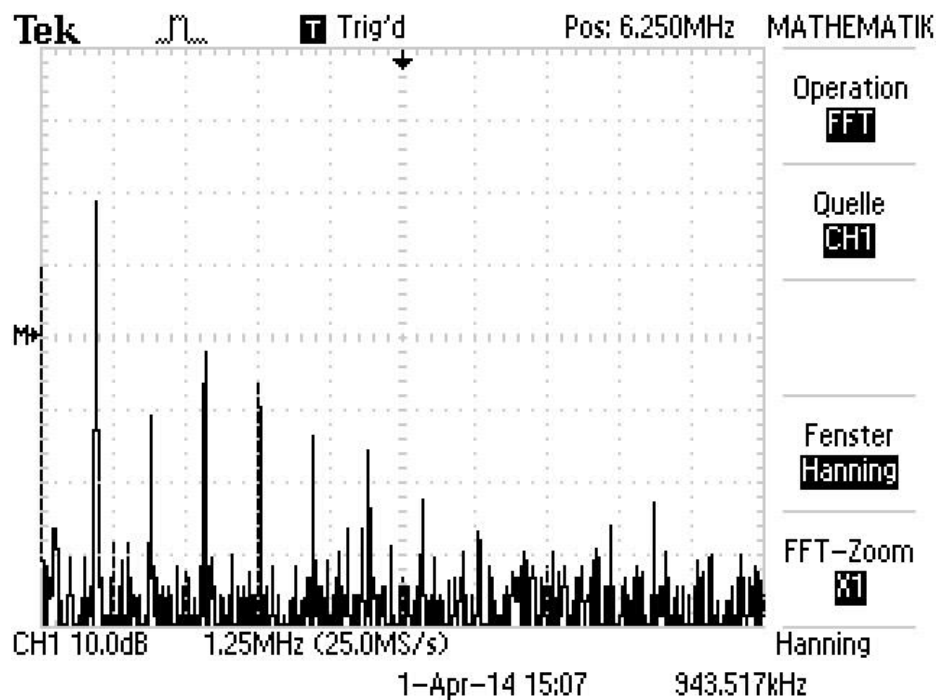


Fig. 21: FFT of the output voltage  $U_a$  at a supply voltage of 3V



## LC-Oscillator

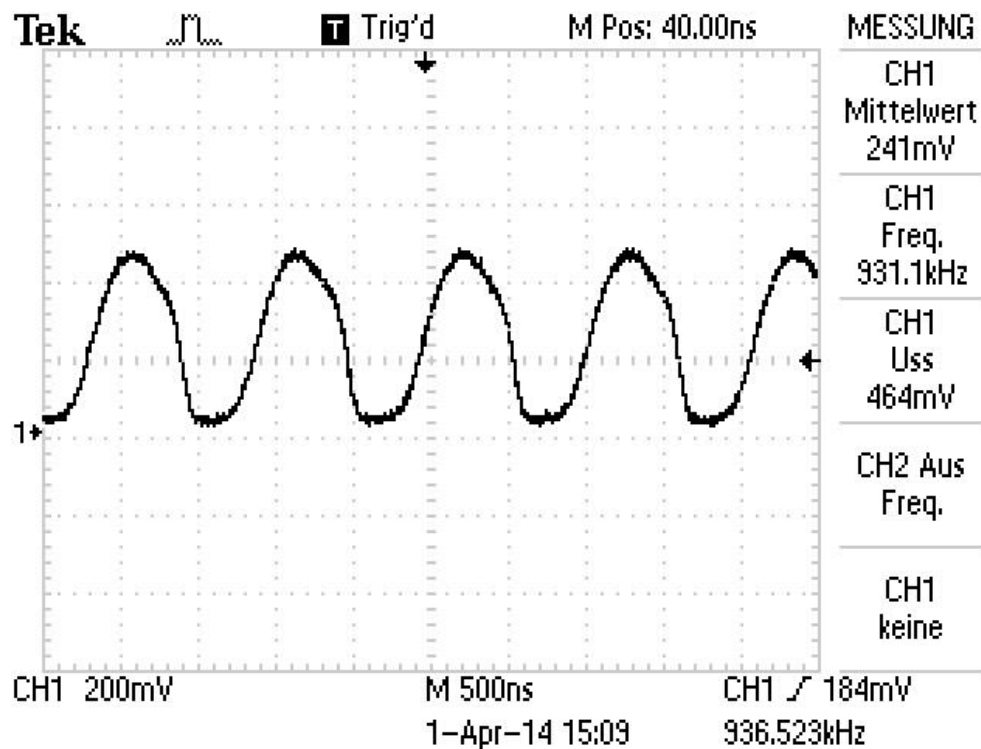


Fig. 22: Voltage course of the output voltage  $U_a$  at a supply voltage of 3,3V

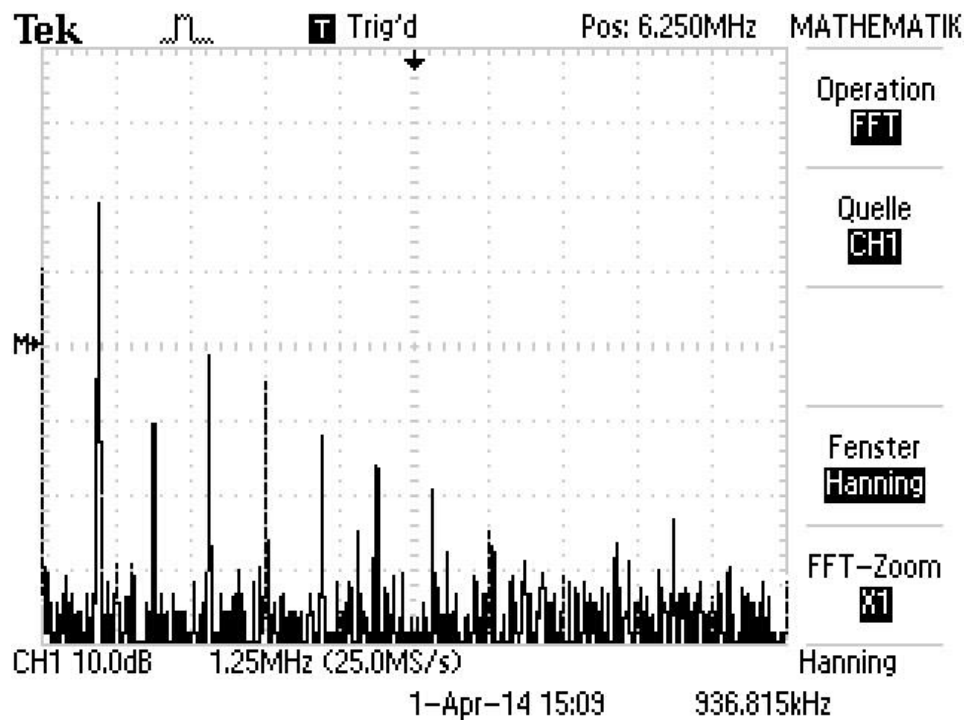


Fig. 23: FFT of the output voltage  $U_a$  at a supply voltage of 3,3V

## LC-Oscillator

### Calculation of the distortion factor:

U1/dBV	U1/V	U2/dBV	U2/V	U3/dBV	U3/V	U4/dBV	U4/V
20	10	-10	0,316	-1	0,891	-25	0,056

$$K = \sqrt{\frac{0,316^2 + 0,891^2 + 0,056^2}{10^2 + 0,316^2 + 0,891^2 + 0,056^2}} = 0,094 \Rightarrow 9,4\%$$

### Comment:

It is apparent that the distortion factor and the offset voltage of U<sub>a</sub> have become smaller, the closer to the supply voltage has risen to 3.3V. After the 4<sup>th</sup> harmonic the FFT is uninteresting. There were no problems in the construction and in the measurement.

## LC-Oscillator

### Task 4:

Design an LC-oscillator with a basic circuit. The oscillator should have a frequency of approximately 900 kHz and a coil with  $22\mu\text{H}$ . Build this circuit on the breadboard. Measure the voltage course and the FFT of the output voltage  $U_a$  with the oscilloscope.

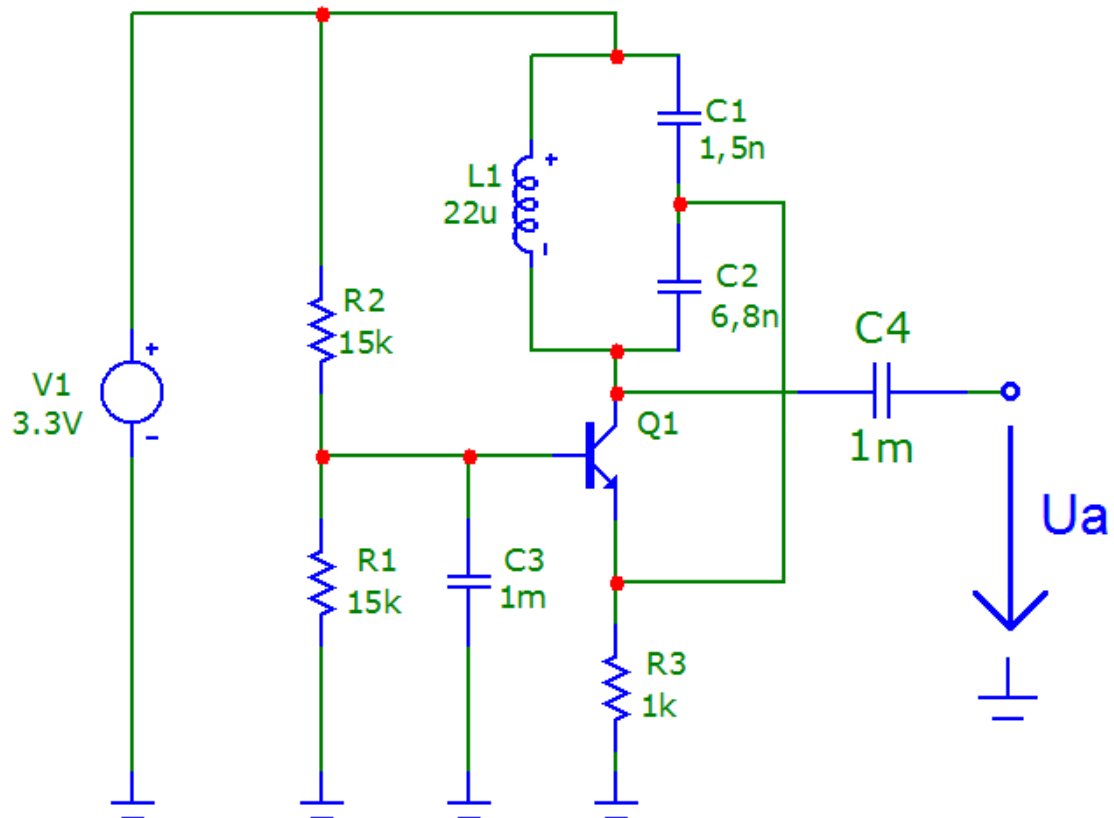


Fig. 24: Basic circuit

### Calculations:

C1 should 5- 10-times be as large as C2

$$\Rightarrow C1 = 6,8\text{n}$$

$$\Rightarrow C2 = 1,5\text{n}$$

$$R3 = 1\text{V} / 1\text{mA} = 1\text{k}\Omega$$

## LC-Oscillator

$$U_{R2} = U_0 * \frac{R1}{R1 + R2}$$

$$U_{R2} = 3,3V * \frac{15k}{15k + 15k} = 1,65V$$

### Measurements:

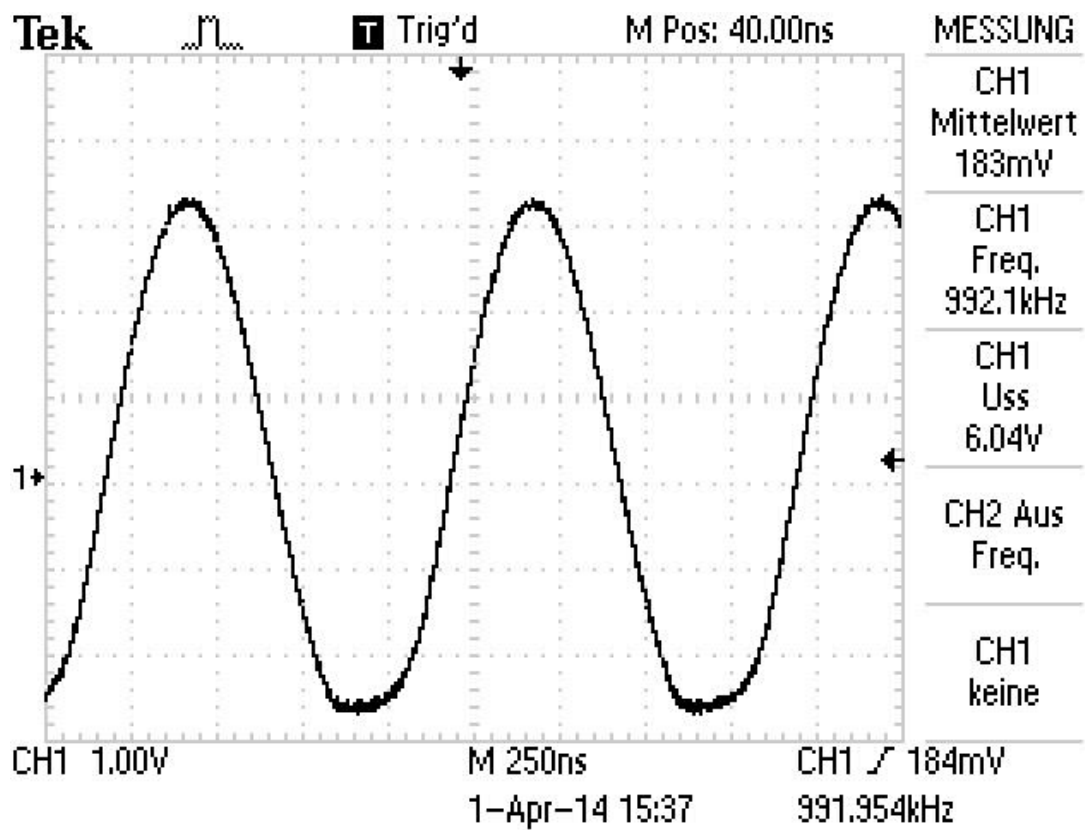


Fig. 25: Voltage course of the output voltage  $U_a$

## LC-Oscillator

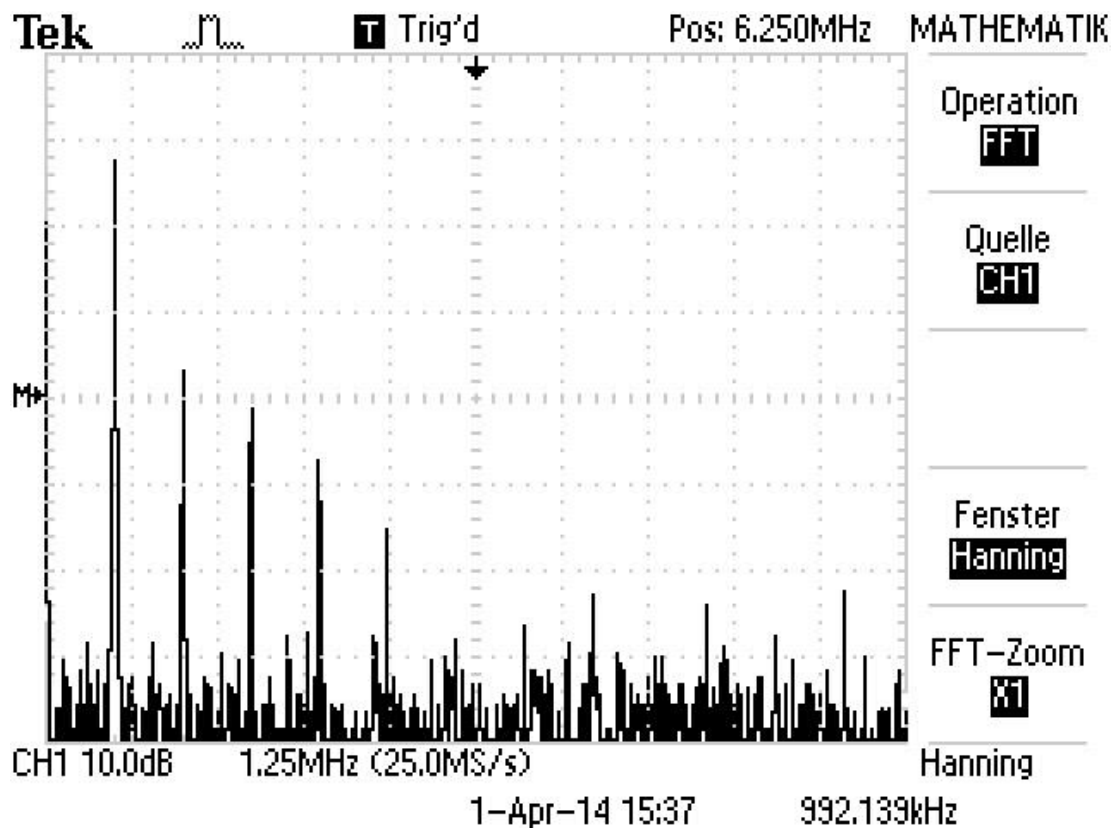


Fig. 26: FFT of the output voltage  $U_a$

### Calculation of the distortion factor:

U1/dBV	U1/V	U2/dBV	U2/V	U3/dBV	U3/V	U4/dBV	U4/V
28	25,12	3	1,41	-1	0,89	-7	0,45

$$K = \sqrt{\frac{1,41^2 + 0,89^2 + 0,45^2}{25,12^2 + 1,41^2 + 0,89^2 + 0,45^2}} = 0,069 \Rightarrow 6,9\%$$

### Comment:

It can be seen that in this circuit, the operating point is well adjusted, because the distortion is very low and the sine look at the most beautiful of all. After the 4<sup>th</sup> harmonic the FFT is uninteresting. There were no problems in the construction and in the measurement.